



MADE EASY

India's Best Institute for IES, GATE & PSUs

Corporate Office (Delhi): 44-A/1 Kalu Sarai (Sarvapriya Vihar), New Delhi-16, **Ph:** 011-45124612, 9958995830

Visit us at: www.madeeasy.in | **E-mail us at:** info@madeeasy.in

Delhi | Hyderabad | Noida | Bhopal | Jaipur | Lucknow | Indore | Pune | Bhubaneswar | Kolkata | Patna

Open Lockdown Period Practice Series for GATE (Also useful for ESE & Other Exams)

EC : ELECTRONICS ENGINEERING

TEST No. - 01 | NETWORK THEORY

Read the following instructions carefully


1. This question paper contains 33 MCQ's & NAQ's. Bifurcation of the questions are given below:

Subjectwise Test Pattern					
Questions	Question Type	No. of Questions	Marks	Total Marks	Negative Marking
1 to 10	Multiple Choice Ques.	10	1	10	0.33
11 to 16	Numerical Answer Type Ques.	6	1	6	None
17 to 26	Multiple Choice Ques.	10	2	20	0.66
27 to 33	Numerical Answer Type Ques.	7	2	14	None
Total Questions : 33		Total Marks : 50		Total Duration : 90 min	

2. Choose the closest numerical answer among the choices given.


Multiple Choice Questions : Q.1 to Q.10 carry 1 mark each

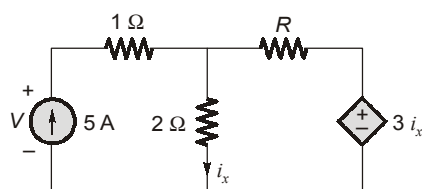Q.1 For the circuit shown below, if the voltage (V) across the current source of 5 A is 25 V, then the value of ' R ' is



- (a) $1\ \Omega$ (b) $2\ \Omega$
(c) $3\ \Omega$ (d) $4\ \Omega$

1. (b)

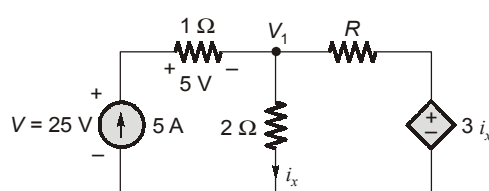

Applying Nodal analysis

$$\Rightarrow \frac{V_1 - 3i_x}{R} + i_x = 5\text{ A}$$


Also $V_1 = 2i_x = 20\text{ V}$
 $i_x = 10\text{ A}$

$$\therefore \frac{2i_x - 3i_x}{R} + i_x = 5\text{ A}$$

$$\frac{20 - 30}{R} + 10 = 5\text{ A}$$

$$\Rightarrow R = 2\ \Omega$$

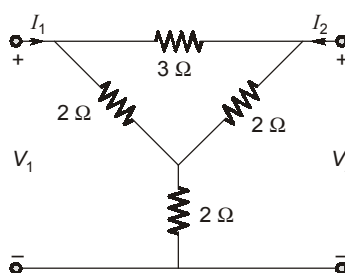Q.2 For the circuit shown below, the admittance parameter matrix $[Y]$ will be




(a) $\begin{bmatrix} \frac{2}{3}\text{ } \Omega & -\frac{1}{2}\text{ } \Omega \\ \frac{1}{2}\text{ } \Omega & \frac{2}{3}\text{ } \Omega \end{bmatrix}$

(b) $\begin{bmatrix} \frac{2}{3}\text{ } \Omega & -\frac{1}{2}\text{ } \Omega \\ -\frac{1}{2}\text{ } \Omega & \frac{2}{3}\text{ } \Omega \end{bmatrix}$


(c) $\begin{bmatrix} \frac{2}{3}\text{ } \Omega & -1\text{ } \Omega \\ -1\text{ } \Omega & \frac{2}{3}\text{ } \Omega \end{bmatrix}$

(d) $\begin{bmatrix} \frac{2}{3}\text{ } \Omega & 1\text{ } \Omega \\ 1\text{ } \Omega & \frac{2}{3}\text{ } \Omega \end{bmatrix}$

2. (b)

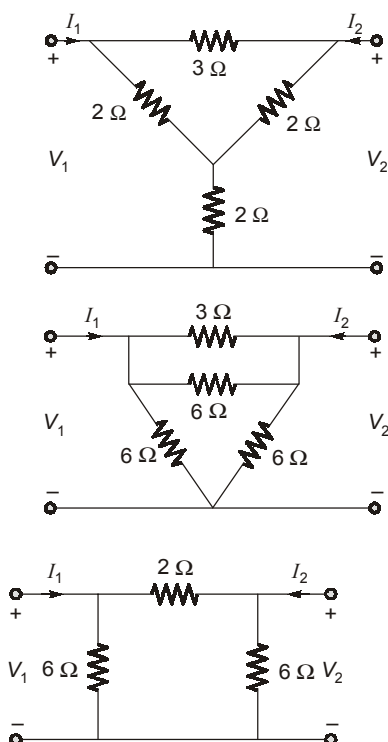

for Π -network

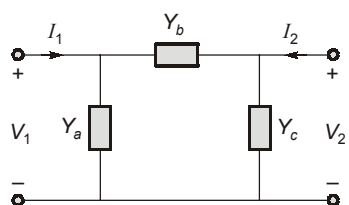

$$\therefore [Y] = \begin{bmatrix} Y_a + Y_b & -Y_b \\ -Y_b & Y_b + Y_c \end{bmatrix}$$

for the given problem, $Y_a = \frac{1}{6} \text{ } \mathcal{U}$

$$Y_b = \frac{1}{2} \text{ } \mathcal{U}$$

$$Y_c = \frac{1}{6} \text{ } \mathcal{U}$$

$$\therefore [Y] = \begin{bmatrix} \frac{2}{3} \text{ } \mathcal{U} & -\frac{1}{2} \text{ } \mathcal{U} \\ -\frac{1}{2} \text{ } \mathcal{U} & \frac{2}{3} \text{ } \mathcal{U} \end{bmatrix}$$

Q.3 If $V(t) = 2\cos(10t)(1 + 2\cos 5t)$ V, then the rms value of $(V(t) + \sqrt{3})$ is

- (a) $3\sqrt{3}$ V (b) $3\sqrt{2}$ V
(c) 3 V (d) 4 V

3. (c)

Let


$$f(t) = V(t) + \sqrt{3}$$

$$\begin{aligned} V(t) &= 2\cos 10t + 4\cos 10t \cdot \cos 5t \\ &= 2\cos 10t + 2\cos 15t + 2\cos 5t \end{aligned}$$

$$f(t) = \sqrt{3} + 2\cos 10t + 2\cos 15t + 2\cos 5t$$

$$\begin{aligned} \text{rms } \{f(t)\} &= \sqrt{(\sqrt{3})^2 + \left(\frac{2}{\sqrt{2}}\right)^2 + \left(\frac{2}{\sqrt{2}}\right)^2 + \left(\frac{2}{\sqrt{2}}\right)^2} \\ &= \sqrt{3 + \frac{4}{2} + \frac{4}{2} + \frac{4}{2}} \\ &= \sqrt{3+6} = \sqrt{9} = 3 \text{ V} \end{aligned}$$

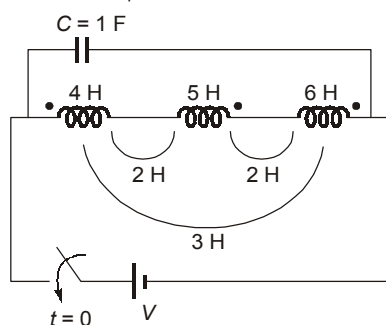Q.4 For the tank circuit shown below, the time period of oscillations is



- (a) 2π seconds (b) 4π seconds
(c) 6π seconds (d) 8π seconds

4. (c)

$$\text{Time period } (T) = \frac{2\pi}{\omega}$$


where

$$\omega = \frac{1}{\sqrt{LC}}$$

thus,

$$T = 2\pi\sqrt{LC}$$

In figure

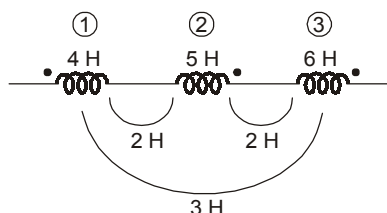


$$\begin{aligned} L_{\text{eq}} &= L_1 + L_2 + L_3 - 2M_{12} + 2M_{23} - 2M_{13} \\ &= 4 + 5 + 6 - 2(2) + 2(2) - 2(3) = 9 \text{ H} \end{aligned}$$

$$C = 1 \text{ F}$$

$$T = 2\pi\sqrt{9} = 6\pi \text{ sec}$$

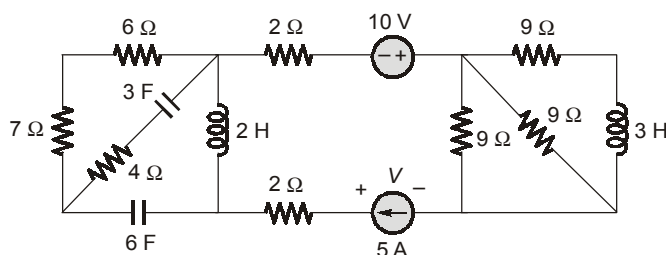
Q.5 For the circuit shown below, the steady state voltage 'V' across the current source is _____?



- (a) 35 V
(b) 25 V
(c) 15 V
(d) none of these

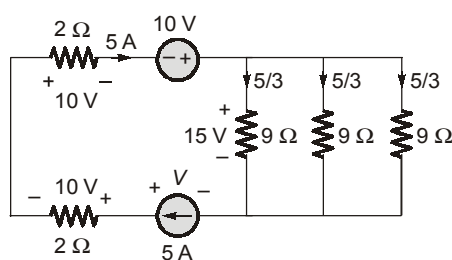5. (b)

The circuit can be redrawn by short circuiting inductor and open circuiting capacitor as DC sources are used.



Applying KVL

$$V - 10 - 10 + 10 - 15 = 0$$

$$V = 25 \text{ V}$$

Q.6 Match **List-I** with **List-II** and select the correct answer using the codes given below the lists:

List-I

- A. $S = 10 \text{ kVA}$, $pf = 0.5$ (lagging)
 B. $S = 13 \text{ kVA}$, $Q = 5 \text{ VAR}$ (capacitive)
 C. $P = 5 \text{ kW}$, $pf = 0.5$ (inductive)

List-II

1. $(5 + j5\sqrt{3}) \text{ kVA}$
 2. $(5 - j5\sqrt{3}) \text{ kVA}$
 3. $(12 + j5) \text{ kVA}$
 4. $(12 - j5) \text{ kVA}$

Codes:

	A	B	C
(a)	1	3	2
(b)	2	4	1
(c)	1	4	1
(d)	2	4	2


6. (c)

for A : $S = 10 \text{ kVA}$; $\cos\phi = pf = 0.5$
 $s = 10[\cos\phi + j\sin\phi] \text{ kVA} = (5 + j5\sqrt{3}) \text{ kVA}$

for B : $S = 13 \text{ kVA}$; $Q = 5 \text{ VAR}$
 $\sin\phi = \frac{Q}{S} = \frac{5}{13} \Rightarrow \cos\phi = \frac{12}{13}$
 $s = 13\left(\frac{12}{13} - j\frac{5}{13}\right) \text{ kVA} = (12 - j5) \text{ kVA}$

for C : $P = 5 \text{ kW}$; $\cos\phi = pf = 0.5$
 $S = \frac{P}{pf} = 10 \text{ kVA}$; $\sin\phi = \frac{\sqrt{3}}{2}$
 $S = 10\left(\frac{1}{2} + j\frac{\sqrt{3}}{2}\right) \text{ kVA} = (5 + j5\sqrt{3}) \text{ kVA}$

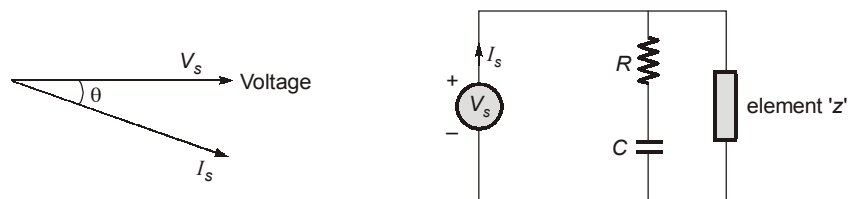
Q.7 For the following phasor diagram of the circuit as shown, the unknown element 'z' is




- (a) R (b) C
 (c) L (d) combination of RC

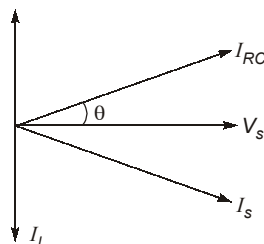7. (c)

Since only L can result in lagging of current with respect to voltage.



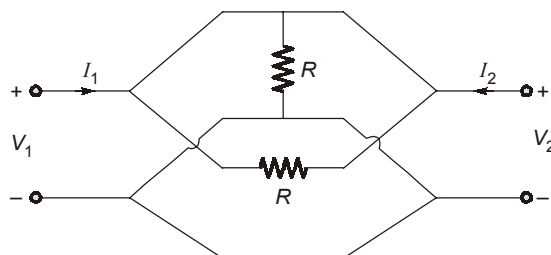Q.8 The Y - parameter matrix of the circuit shown below is



(a) $\begin{bmatrix} 2R & 2R \\ 2R & 2R \end{bmatrix}$

(b) $\begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix}$

(c) $\begin{bmatrix} \frac{1}{2R} & \frac{1}{2R} \\ \frac{1}{2R} & \frac{1}{2R} \end{bmatrix}$

(d) doesn't exist

8. (d)


$$[Y] = [Y_1] + [Y_2]$$

$$[Z_1] = \begin{bmatrix} R & R \\ R & R \end{bmatrix}$$

Since determinant is zero,
therefore 'Y' parameter doesn't exist.

$$[Y] = [Z]^{-1} = \frac{1}{0} \begin{bmatrix} R & R \\ R & R \end{bmatrix} \Rightarrow \text{Not possible}$$

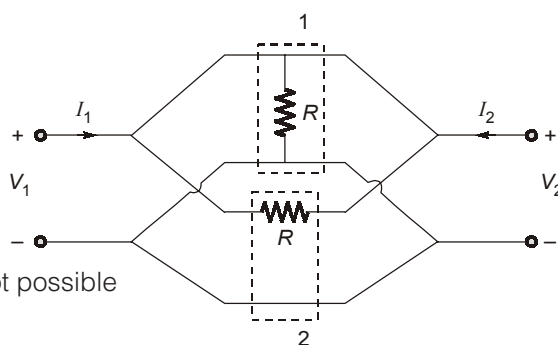as $[Y_1]$ doesn't exist, $[Y]$ also doesn't exist.



Q.9 The unit of $\frac{R}{2} \sqrt{\frac{L}{C}}$ is

(a) Ω

(b) Ω^2

(c) no unit

(d) $\Omega \text{H rad}$

9. (b)


$$\frac{R}{2} \sqrt{\frac{L}{C}} \Rightarrow \frac{R}{2} \sqrt{\frac{L\omega}{C\omega}} = \frac{R}{2} \sqrt{X_L X_C}$$

Unit of R_1 is Ω

Unit of ' X_L ' and ' X_C ' is Ω

$$\text{Unit of } \frac{R}{2} \sqrt{\frac{L}{C}} \text{ is } \Omega \times \sqrt{\Omega \times \Omega} \Rightarrow (\Omega)^2$$

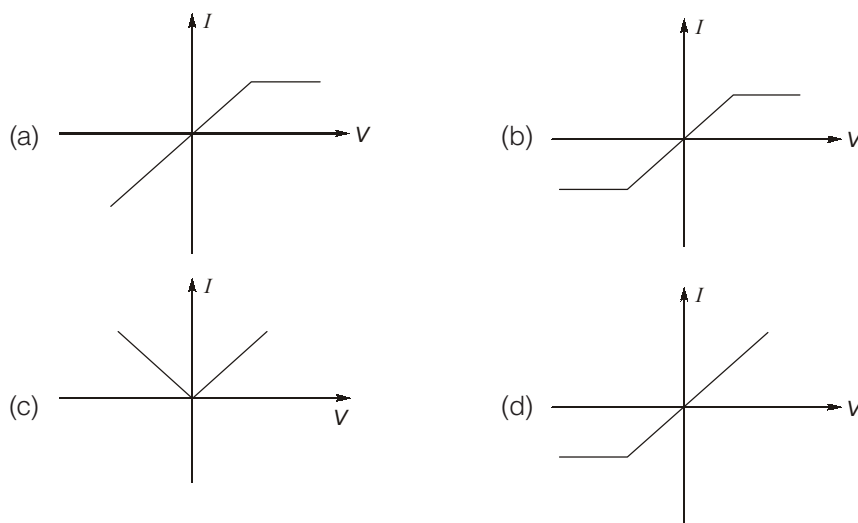Q.10 Which of the following graphs, represents an ACTIVE element.



10. (c)

Numerical Answer Type Questions : Q. 11 to Q. 16 carry 1 mark each

Q.11 A parallel R, L, C circuit has $R = 2 \text{ k}\Omega$, $L = 240 \text{ mH}$, $C = 54 \text{ }\mu\text{F}$. The quality factor of the circuit at resonance is _____.

11. (30)

For parallel resonant circuit

$$Q_0 = R\sqrt{\frac{C}{L}}$$


$$Q_0 = 2000\sqrt{\frac{54 \times 10^{-6}}{240 \times 10^{-3}}}$$

$$Q_0 = 2000\sqrt{\frac{9}{4} \times 10^{-4}}$$


$$Q_0 = \frac{2000}{100} \times \frac{3}{2}$$

$$Q_0 = 30$$

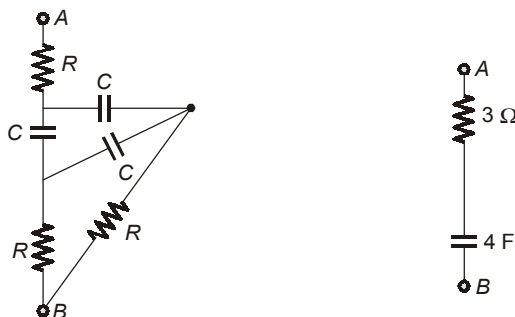Q.12 If both the circuits shown below are equivalent, then the value of RC is _____ sec.



12. (4)

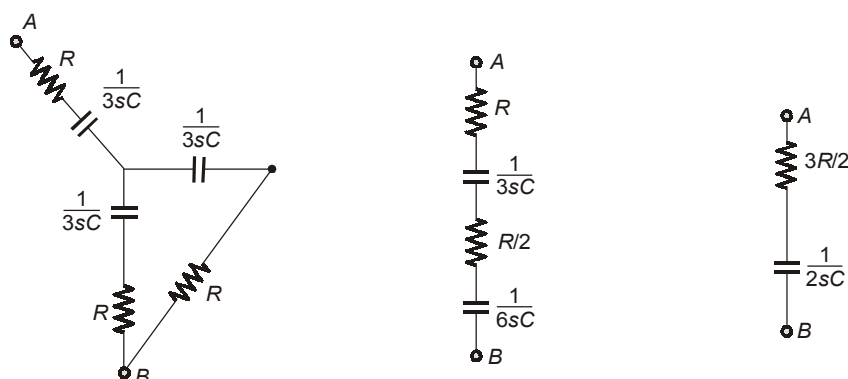

comparing with given diagram

$$R_{eq} = 3\Omega = \frac{3R}{2} \text{ and } C_{eq} = 4F = 2C$$


so,

$$R = 2\Omega$$

$$C = 2F$$

$$RC = 4 \text{ sec}$$

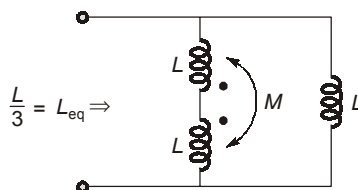Q.13 If L_{eq} of the circuit shown below is $\left(\frac{L}{3}\right)$ H, then the coupling coefficient (k) is _____.



13. 0.75 (0.70 to 0.80)

$$L_{eq} = (L + L - 2M) \parallel L$$

Also


$$M = k\sqrt{L_1 L_2} = M = k\sqrt{L^2} = kL$$

$$L_{eq} = (L + L - 2kL) \parallel L$$


$$\frac{L}{3} = \frac{(2L - 2kL) \times L}{2L - 2kL + L}$$

on solving, we get

$$k = 0.75$$

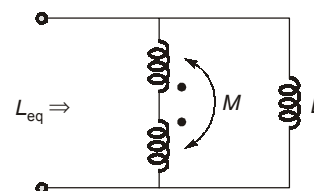


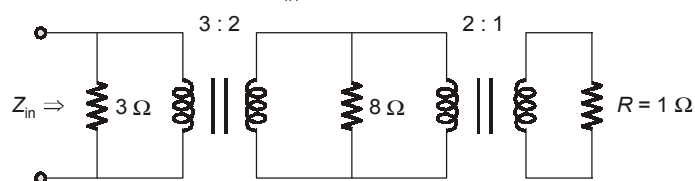Q.14 For the circuit shown below, the value of Z_{in} is _____ Ω .




14. (2)

The circuit can be modified as

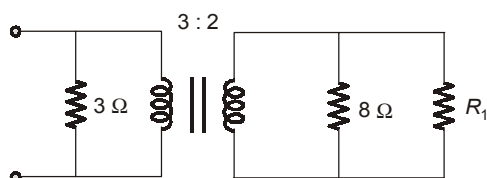

$$R_1 = \left(\frac{2}{1}\right)^2 \times 1 \Omega = 4 \Omega$$
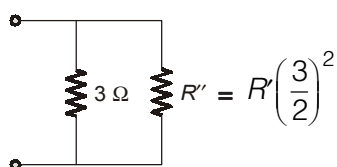
$$R' = 4 \parallel 8 = \frac{4 \times 8}{12} = \frac{8}{3} \Omega$$




$$R'' = \frac{8}{3} \times \frac{9}{4} = \frac{72}{12} = 6 \Omega$$

$$Z_{in} = R'' \parallel 3 \Omega = 6 \Omega \parallel 3 \Omega$$

$$Z_{in} = 2 \Omega$$

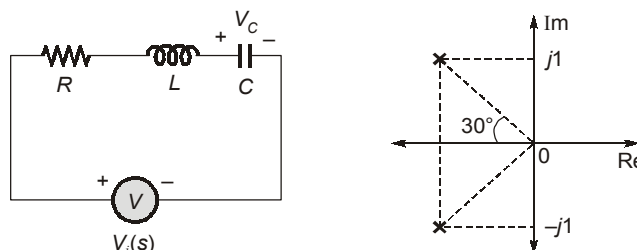Q.15 For a series RLC circuit shown below, the poles of the transfer function $\left(\frac{V_C(s)}{V_i(s)}\right)$ are plotted as shown. If

$\frac{R}{C} = 2\sqrt{3}$, then the value of R is _____ ohms.




15. 1.73 (1.60 to 1.80)

$$\frac{V_C(s)}{V_i(s)} = \frac{\frac{1}{sC}}{sL + R + \frac{1}{sC}} = \frac{\frac{1}{sC}}{\frac{s^2LC + sRC + 1}{sC}} = \frac{1}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

The characteristic equation : $s^2 + \frac{R}{L}s + \frac{1}{LC}$... (i)

as per graph

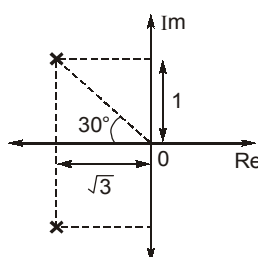

$$C(s) = (s + \sqrt{3} + j1)(s + \sqrt{3} - j1)$$

$$\begin{aligned} C(s) &= s^2 + 2\sqrt{3}s + 3 + 1 \\ &= s^2 + 2\sqrt{3}s + 4 \end{aligned} \quad \dots (ii)$$

On comparison $\frac{R}{L} = 2\sqrt{3}$... (iii)

$$\frac{1}{LC} = 4 \quad \dots (iv)$$

$$\frac{R}{C} = 2\sqrt{3} \quad \text{given} \quad \dots (v)$$

from (ii) and (iii)

$$\frac{\frac{R}{L}}{\frac{1}{LC}} = RC = \frac{\sqrt{3}}{2}$$


$$\frac{R}{C} = 2\sqrt{3}$$

multiplying $R^2 = \frac{\sqrt{3}}{2} \times 2\sqrt{3} = 3$


$$R = \sqrt{3}$$

$$R = 1.732 \Omega$$

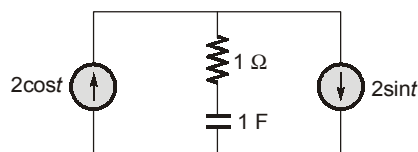Q.16 In the circuit shown below, the average power dissipated by $1\ \Omega$ resistor is _____ Watts.



16. (4)

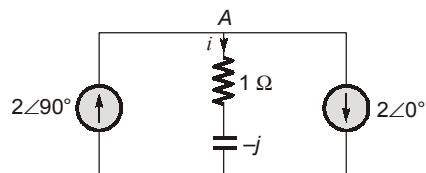

Applying KCL at node A

$$i = 2\angle 90^\circ - 2\angle 0^\circ$$

$$i = 2j - 2 = -2 + 2j$$

$$i = 2\cos t - 2\sin t$$

$$p(t) = i^2 R$$

$$p(t) = (2\cos t - 2\sin t)^2 \times 1$$


$$p(t) = 4\cos^2 t + 4\sin^2 t - 8\sin t \cos t$$

$$p(t) = 4 - 4\sin 2t$$

$$p_{\text{avg}} = 4 \text{ Watts}$$




Multiple Choice Questions : Q.17 to Q.26 carry 2 marks each

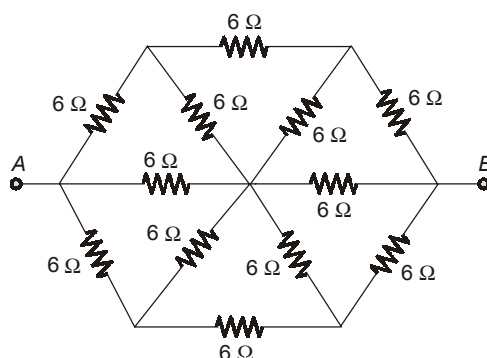Q.17 The equivalent resistance between the terminals A and B is




- (a) 1.2Ω (b) 3.6Ω
(c) 4.8Ω (d) 6Ω


17. (c)

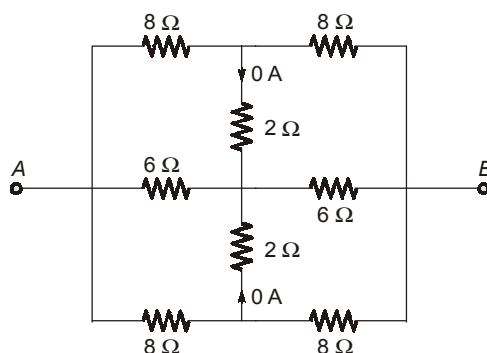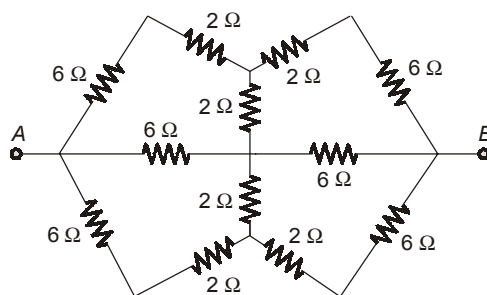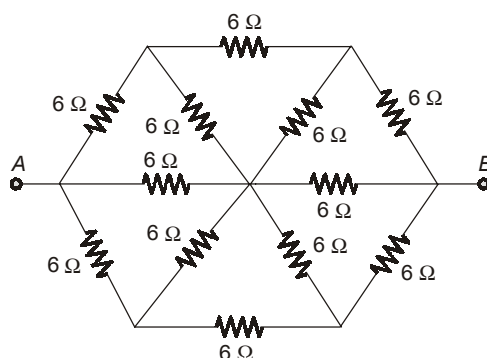

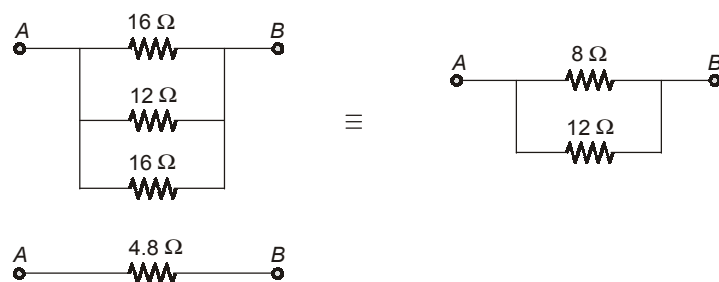Since two Wheatstone bridges are connected parallelly, no current flows through $2\ \Omega$ resistors.



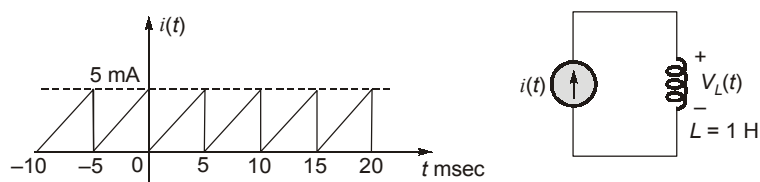Q.18 A periodic sawtooth current wave is passed through an inductor of 1 H as shown below. The value of $V_L(t)$ at $t = 3\text{ msec}$ is




- (a) 1 V (b) 2 V
(c) 3 V (d) 4 V

18. (a)


$$V_L(t) = \frac{L di(t)}{dt} = \frac{di(t)}{dt} \quad \because L = 1\text{ H}$$

Differentiating $i(t)$, we get

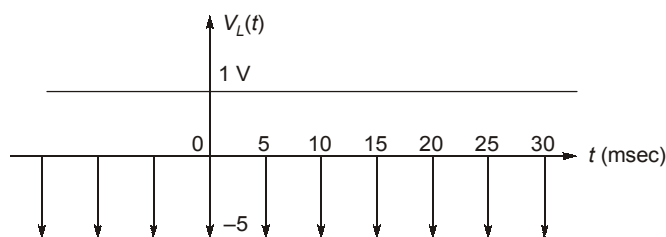


$V_L(t)$ at $t = 3\text{ msec} = 1\text{ V}$

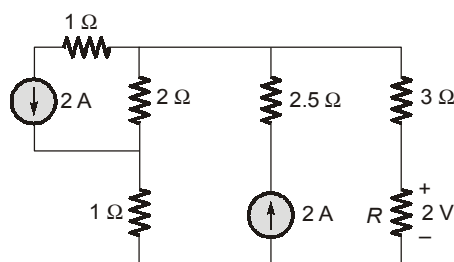Q.19 For the circuit shown below, the value of R (in ohms) is



- (a) 2
(b) 4
(c) 6
(d) none of these

19. (d)

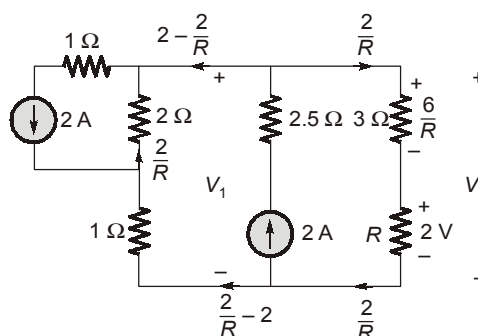

$$V_1 = -\frac{4}{R} - 1\left(\frac{2}{R} - 2\right)$$

$$V_1 = -\left(\frac{4}{R} + \frac{2}{R} - 2\right) = -\left(\frac{6}{R} - 2\right) = 2 - \frac{6}{R}$$

$$V_2 = \frac{6}{R} + 2$$


$$\Rightarrow V_1 = V_2 \quad (\because \text{for parallel branches voltage is same})$$

$$2 - \frac{6}{R} = \frac{6}{R} + 2$$

$$\frac{12}{R} = 0$$

$$R = \infty \quad (\text{open circuit})$$


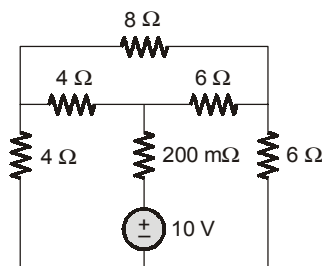
Q.20 The power absorbed by $200\text{ m}\Omega$ resistance in the given circuit is



- (a) 0.2 Watts
(b) 0.4 Watts
(c) 0.6 Watts
(d) 0.8 Watts

20. (d)


The circuit can be redrawn as

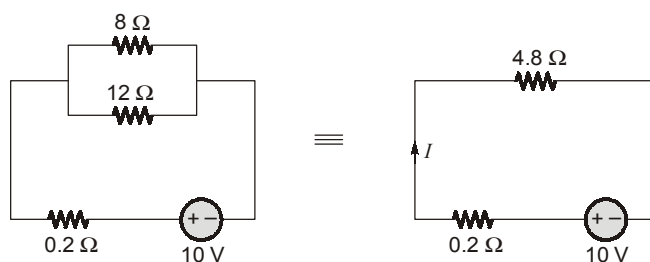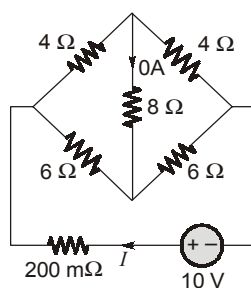

$$I = \frac{10}{5} = 2\text{ A}$$

$$\begin{aligned} P_{\text{absorbed}} &= (0.2)(2)^2 \\ &= 0.2 \times 4 = 0.8\text{ Watts} \end{aligned}$$

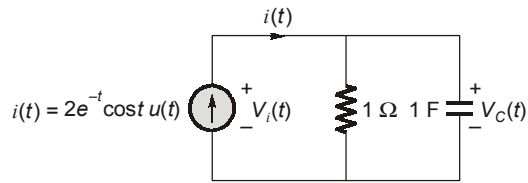
Q.21 For the circuit shown below, if $i(t) = 2e^{-t} \cos t u(t)$ A, then the voltage across the capacitor $V_C(t)$ will be



- (a) $2e^{-t} \cos t u(t)$ V
(c) $e^{-t} \sin t u(t)$ V

- (b) $e^{-t} \cos t u(t)$ V
(d) $2e^{-t} \sin t u(t)$ V

21. (d)

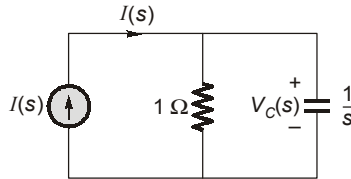


$$V_C(s) = I(s) \times \frac{1}{1 + \frac{1}{s}} \times \frac{1}{s} = I(s) \times \frac{1}{s+1}$$

$$I(s) = \frac{2(s+1)}{(s+1)^2 + 1}$$

$$V_C(s) = \frac{2(s+1)}{(s+1)^2 + 1} \times \frac{1}{1+s} = \frac{2}{(s+1)^2 + 1}$$

$$v_C(t) = 2e^{-t} \sin t u(t) \text{ V}$$

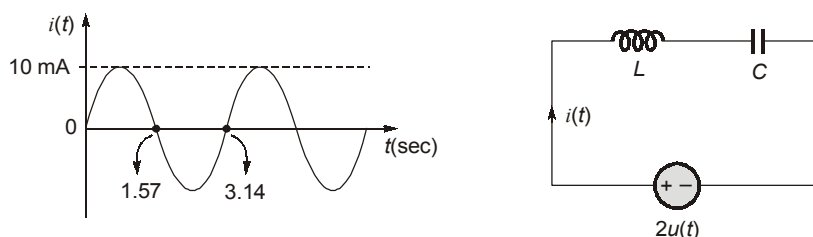Q.22 The current flowing through a series LC circuit excited by a step voltage is sinusoidal as shown below. Find the values of L and C




- (a) $L = 10 \text{ H}, C = 25 \text{ mF}$ (b) $L = 100 \text{ H}, C = 2.5 \text{ mF}$
(c) $L = 100 \text{ H}, C = 25 \text{ mF}$ (d) $L = 10 \text{ H}, C = 2.5 \text{ mF}$

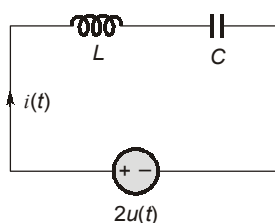22. (b)

from the given diagram

$$i(t) = 10 \sin 2t u(t) \text{ mA} \quad \dots(i)$$



$$\Rightarrow I(s) = \frac{\frac{2}{s}}{sL + \frac{1}{sC}}$$

$$I(s) = \frac{\frac{2}{s}}{\frac{s^2 LC + 1}{sC}} = \frac{2C}{s^2 LC + 1}$$

$$I(s) = \frac{\frac{2}{L}}{s^2 + \frac{1}{LC}} \quad \dots(ii)$$


From equation (i) $I(s) = 10 \times 10^{-3} \left(\frac{2}{s^2 + 4} \right) \quad \dots(iii)$

$$\therefore \frac{1}{LC} = 4 \quad \text{and} \quad \frac{2}{100} = \frac{2}{L}$$

$$L = 100 \text{ H}$$

$$C = 2.5 \text{ mF}$$

Q.23 Consider the network shown below.

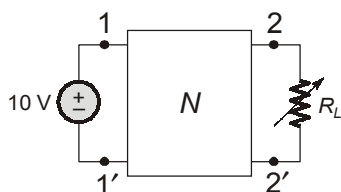


If the hybrid parameter matrix of the Network 'N' is $[h] = \begin{bmatrix} 3 & 5 \\ 1 & 2 \end{bmatrix}$, then the maximum power that can be transferred to R_L is ____.

- (a) 8.33 W (b) 16.66 W
(c) 25 W (d) 50 W

23. (a)

to determine V_{th} :

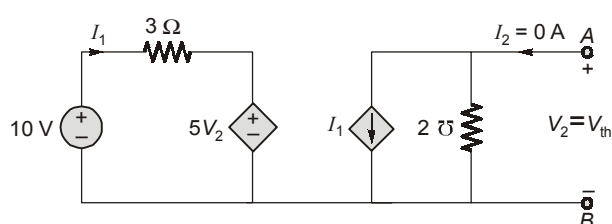

$$I_1 = \frac{10 - 5V_2}{3} = \frac{10 - 5V_{th}}{3}$$

$$V_{th} = -\frac{I_1}{2} = \frac{5V_{th} - 10}{6}$$

$$6V_{th} = 5V_{th} - 10$$

$$V_{th} = -10 \text{ V}$$


to determine R_{th} :

$$I_2 = 2V_2 + I_1$$

$$1 \text{ A} = 2V_2 + I_1$$

$$0 = 3I_1 + 5V_2$$

$$I_1 = -\frac{5}{3}V_2$$

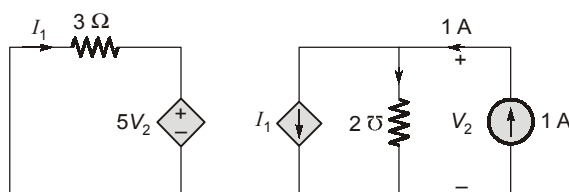


$$1 \text{ A} = 2V_2 - \frac{5}{3}V_2$$

$$V_2 = 3 \text{ V}$$

$$R_{th} = \frac{V_2}{1 \text{ A}} = 3 \Omega$$

$$P_{L \max} = \frac{V_{th}^2}{4R_{th}} = \frac{100}{12} \text{ W} = 8.33 \text{ W}$$

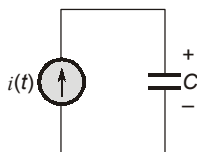Q.24 If the maximum energy stored in a capacitor shown below is finite, then the possible current source charging the capacitor is



- (a) Impulse
(b) Ramp
(c) Unit step
(d) Parabolic

24. (a)

Maximum energy stored in a capacitor is given as

$$E_{\max} = \frac{1}{2} C V_{\max}^2$$

option (a) Impulse current

$$i(t) = \frac{C dv}{dt}$$

$$\Rightarrow V_C(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt$$

$$i(t) = \delta(t)$$

$$V_C(t) = \frac{1}{C} u(t)$$

$$\Rightarrow V_{\max} = \frac{1}{C}$$

$$E_{\max} = \frac{1}{2} C \left(\frac{1}{C} \right)^2 = \frac{1}{2C}$$

option (b) Ramp

$$V_C(t) = \frac{1}{C} \int \text{Ramp} = \text{parabolic}$$

$$V_{\max} = \infty$$

option (c) unit step

$$V_C(t) = \frac{1}{C} \int_{-\infty}^t u(t) dt = \frac{1}{C} r(t) = \frac{1}{C} t u(t)$$

$$V_{\max} = \infty$$

option (d) parabolic

$$V_{\max} = \infty$$


Thus option (a) is the correct choice.

- Q.25** If $V_{rms} = 120\angle 60^\circ$ and $Z = 60 - j80$, then the complex power 'S' is
 (a) $(90 - j120)$ VA (b) $(86.4 + j115.2)$ VA
 (c) $(86.4 - j115.2)$ VA (d) $(90 + j120)$ VA

25. (c)

$$\text{Complex power 'S'} = \frac{|V_{rms}|^2}{Z^*} = \frac{|120|^2}{60 + j80} = \frac{14400 \times (60 - j80)}{100 \times 100} = 1.44(60 - j80) \\ = (86.4 - j115.2) \text{ VA}$$

Q.26

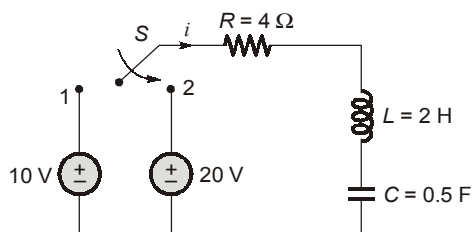


If the switch is at position '1' for a long time and at $(t = 0)$ it is moved to position '2', then the current $i(t)$ for $t > 0$ will be


- (a) $(5e^{-t} + 25e^t)$ A (b) $(5 + 25te^{-t})$ A
 (c) $(5te^{-t})$ A (d) $(25te^{-t} + 5)$ A

26. (c)

At $(t = 0^-)$

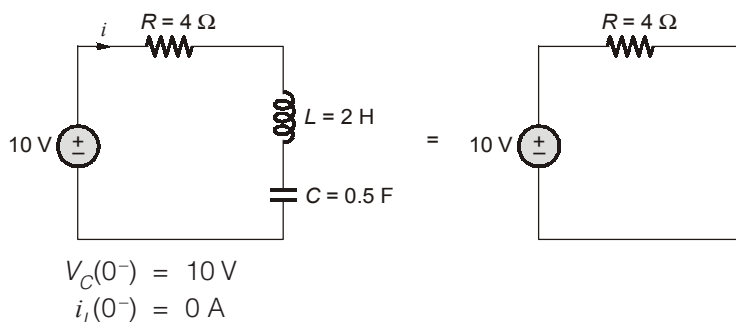

At $(t = 0^+)$

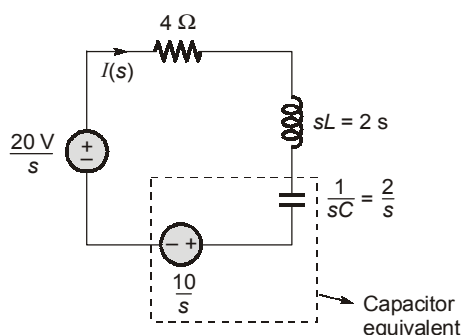

$$I(s) = \frac{10/s}{4 + 2s + \frac{2}{s}} = \frac{10/s}{\frac{4s + 2s^2 + 2}{s}} = \frac{10}{2(s^2 + 2s + 1)}$$

$$I(s) = \frac{5}{(s+1)^2}$$

$$i(t) = 5te^{-t} u(t) \text{ A}$$


Numerical Answer Type Questions : Q.27 to Q.33 carry 2 marks each

Q.27 For the circuit shown below, the current $i(t)$ and the voltage $v_L(t)$ are given as respectively

$$i(t) = A(1 - e^{-Bt}) u(t) \text{ A}$$

$$v_L(t) = Ce^{-Bt} u(t) \text{ V}$$

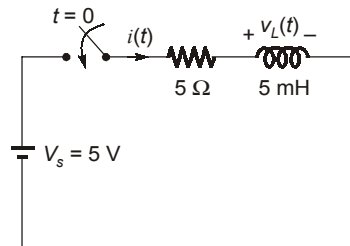The value of expression $\frac{AB}{C}$ is _____.



27. (200)

For a series RL circuit with DC excitation,

$$i(t) = \frac{V_s}{R} \left(1 - e^{-\frac{Rt}{L}} \right) u(t) \text{ A}$$

$$v(t) = V_s \left(e^{-\frac{Rt}{L}} \right) u(t) \text{ A}$$

$$A = \frac{V_s}{R}$$


$$B = \frac{R}{L}$$

$$C = V_s$$

$$\frac{AB}{C} = \frac{\frac{V_s}{R} \times \frac{R}{L}}{V_s} = \frac{1}{L}$$


$$= \frac{1}{5 \times 10^{-3}} = 200$$

Q.28 Consider the circuit shown below.

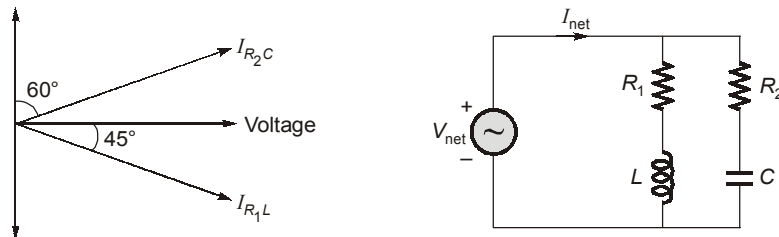

If $L = C$, then the minimum value of $R_1 + R_2$ is _____ Ω .

28. 2.63 (2.50 to 2.80)

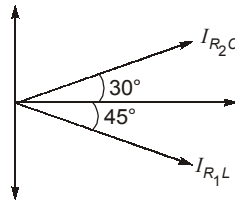

From phasor, we can write

$$\tan 30^\circ = \frac{X_C}{R_2}$$

$$\Rightarrow R_2 = X_C \sqrt{3} = \frac{\sqrt{3}}{\omega C}$$

$$\tan 45^\circ = \frac{X_L}{R_1}$$

$$\Rightarrow R_1 = X_C = \omega L$$

$$R_1 R_2 = \frac{\sqrt{3}}{\omega C} \times \omega L = \frac{L}{C} \sqrt{3}$$

$$R_1 R_2 = \sqrt{3} = 1.732$$

we know

$$\frac{R_1 + R_2}{2} \geq \sqrt{R_1 R_2}$$


as arithmetic mean \geq geometric mean ; (for non-negative real numbers)

$$R_1 + R_2 \geq 2\sqrt{\sqrt{3}}$$

$$R_1 + R_2 \geq 2(3)^{1/4}$$

Minimum value of $R_1 + R_2 = 2.63 \Omega$

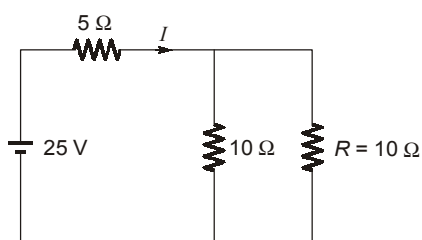
Q.29 For the circuit shown below, if R is increased by 10%, then the change in current I will be _____ mA.




29. -58.14 (-58.50 to -57.50)

$$I_{\text{initial}} = 2.5 \text{ A}$$

$$I_1 = 1.25 \text{ A}$$

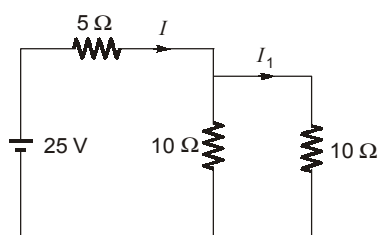

Using compensation theorem

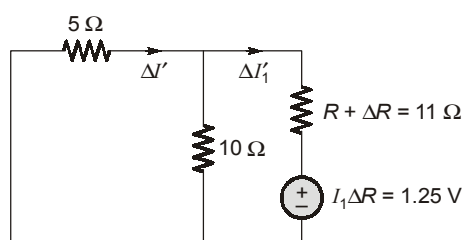


$$\Delta R = 1 \Omega$$


$$-\Delta I_1' = \frac{1.25}{(10 \parallel 5) + 11} = \frac{1.25}{14.33} = 0.08721 \text{ A}$$

$$\Delta I' = -\Delta I_1' \times \frac{10}{15} = \frac{-2}{3} \Delta I_1' = -0.05814 \text{ A} = -58.14 \text{ mA}$$

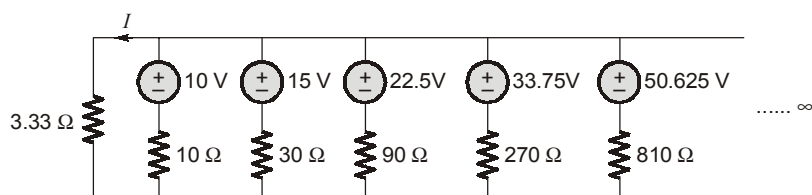Q.30 For the circuit shown below, the current I is _____ Amp.



30. 1.33 (1.30 to 1.40)

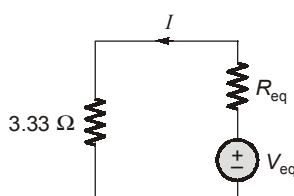

Applying Millman's Theorem

$$\frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{30} + \frac{1}{90} + \dots$$

$$\frac{1}{R_{eq}} = \frac{1}{10} \left(1 + \frac{1}{3} + \frac{1}{9} + \dots \right)$$


$$\frac{1}{R_{eq}} = \frac{1}{10} \left(\frac{1}{1 - \frac{1}{3}} \right) = \frac{3}{10 \times 2} = \frac{3}{20}$$

$$R_{eq} = \frac{20}{3} \Omega$$

$$V_{eq} = \frac{\frac{E_1}{R_1} + \frac{E_2}{R_2} + \frac{E_3}{R_3} + \dots}{\frac{1}{R_{eq}}}$$

$$= \frac{1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \dots}{\frac{3}{20}} = \frac{1 - \frac{1}{2}}{\frac{3}{20}} = \frac{20}{3} \times 2$$


$$V_{eq} = \frac{40}{3} \text{ V}$$

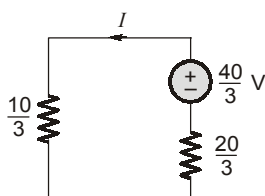

$$I = \frac{\frac{40}{3}}{\frac{20}{3} + \frac{10}{3}} = \frac{\frac{40}{3}}{\frac{30}{3}} = \frac{4}{3} \text{ A}$$

$$I = 1.33 \text{ A}$$


Q.31 For the circuit shown below,

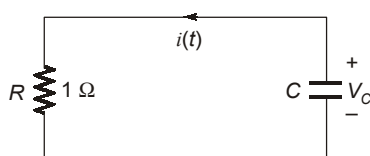

If $i(0^-) = 5 \text{ A}$ and $i(t)|_{t=3 \text{ msec}} = 2.5 \text{ A}$, then the value of C is _____ mF.

31. 4.328 (4.20 to 4.50)

at $t = 0^-$:

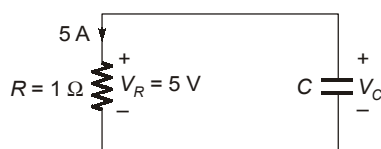

$$\begin{aligned} \Rightarrow V_R - V_C &= 0 \\ \Rightarrow V_R &= V_C = 5 \text{ V} \\ \text{thus } V_C(0^-) &= 5 \text{ V} = V_C(0^+) \\ \text{Taking Laplace domain} \end{aligned}$$

$$I(s) = \frac{\frac{5}{s}}{1 + \frac{1}{sC}}$$

$$I(s) = \frac{\frac{5}{s}}{\frac{sC + 1}{sC}}$$

$$I(s) = \frac{5C}{1 + sC} = \frac{5}{s + \frac{1}{C}}$$

$$\begin{aligned} i(t) &= 5e^{-t/C} u(t) \\ i(t)|_{3 \text{ msec}} &= 2.5 \end{aligned}$$

$$2.5 = 5e^{-\frac{3 \times 10^{-3}}{C}}$$


$$\frac{1}{2} = e^{-\frac{3 \times 10^{-3}}{C}}$$

$$-\ln 2 = \frac{-3 \times 10^{-3}}{C}$$


$$C = \frac{3 \times 10^{-3}}{\ln 2}$$

$$C = \frac{3}{\ln 2} \text{ mF}$$

$$C = 4.328 \text{ mF}$$

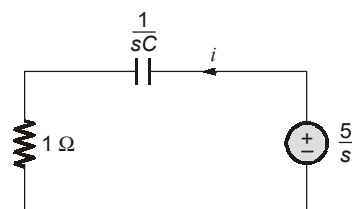

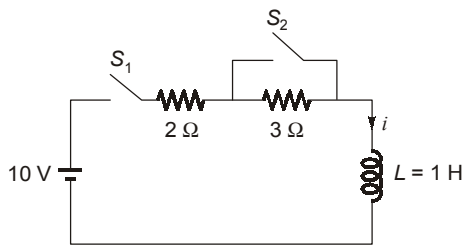Q.32 For the circuit shown below, the switch S_1 and S_2 are open for a long time. At $t = 0$, S_1 is closed, while S_2 is open. At $t = 2$ sec, S_2 is also closed.




The value of current i at $t = 3$ sec is _____ A.
(Take appropriate approximations).

32. 4.594 (4.40 to 4.70)

At $(t = 0^-)$, both the switches are opened.

L is initially uncharged $i_L(0^-) = 0$

At $(t = 0^+)$

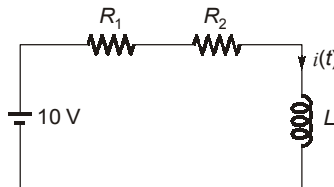

$$i(t) = i(\infty) + (i(0^+) - i(\infty)) e^{-\frac{R_{eq} t}{L_{eq}}}$$

$$R_{eq} = 5 \Omega$$

$$L_{eq} = 1 \text{ H}$$

$$i(0^+) = 0 \text{ A}$$

$$i(t) = 2 + (0 - 2)e^{-\frac{5t}{1}} \text{ A ; for } t > 0$$

At $(t = 2^-)$


$$i(2^-) = 2 - 2e^{-\frac{10}{1}} \text{ A}$$

$$i(2^-) \approx 2 \text{ A}$$

At $(t = 2^+)$

$$i(2^-) = i(2^+) = 2 \text{ A}$$

for $t > 2$ sec

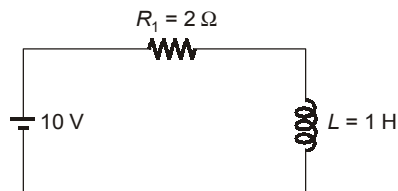


$$i(t) = i(\infty) + (i(2^+) - i(\infty)) e^{-\frac{R_1(t-2)}{L}} ; \text{ for } t > 2$$

$$i(t)|_{t=3s} = 5 + (2 - 5)e^{-\frac{2}{1}(3-2)} = 5 - 3e^{-2}$$

$$= 4.594 \text{ A}$$

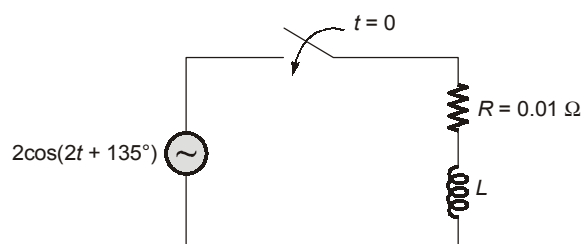Q.33 If the circuit shown below has zero transient response, then the value of L is _____ mH.



33. (5)

$$V = 2\cos(2t + 135^\circ)$$

In AC transients, for transient free response

$$\theta = \tan^{-1}\left(\frac{\omega L}{R}\right) + \frac{\pi}{2}$$

$$135^\circ = \tan^{-1}\left(\frac{\omega L}{R}\right) + 90^\circ$$

$$\tan(45^\circ) = \frac{\omega L}{R}$$

\Rightarrow

$$\omega L = R$$

\Rightarrow

$$R = 2L$$

$$\frac{R}{2} = L = \frac{0.01}{2}$$

$$L = 5 \text{ mH}$$

○○○○