



# MADE EASY

India's Best Institute for IES, GATE & PSUs

**Corporate Office (Delhi):** 44-A/1 Kalu Sarai (Sarvapriya Vihar), New Delhi-16, **Ph:** 011-45124612, 9958995830

**Visit us at:** [www.madeeasy.in](http://www.madeeasy.in) | **E-mail us at:** [info@madeeasy.in](mailto:info@madeeasy.in)

Delhi | Hyderabad | Noida | Bhopal | Jaipur | Lucknow | Indore | Pune | Bhubaneswar | Kolkata | Patna

## Lockdown Period Open Practice Test Series (Also useful for ESE & Other Exams)

**EC : ELECTRONICS ENGINEERING**

**TEST No. - 10 | DIGITAL ELECTRONICS**

**Read the following instructions carefully**


1. This question paper contains 33 MCQ's & NAQ's. Bifurcation of the questions are given below:

Subjectwise Test Pattern					
Questions	Question Type	No. of Questions	Marks	Total Marks	Negative Marking
1 to 10	Multiple Choice Ques.	10	1	10	0.33
11 to 16	Numerical Answer Type Ques.	6	1	6	None
17 to 26	Multiple Choice Ques.	10	2	20	0.66
27 to 33	Numerical Answer Type Ques.	7	2	14	None
Total Questions : 33		Total Marks : 50		Total Duration : 90 min	

2. Choose the closest numerical answer among the choices given.

**Multiple Choice Questions : Q.1 to Q.10 carry 1 mark each**

 **Q.1** The circuit shown below is used to implement the function  $z = f(A, B) = \bar{A} + B$ . The values of  $P$  and  $Q$  are



- (a)  $P = A, Q = B$  (b)  $P = B, Q = \bar{A}$   
(c)  $P = \bar{B}, Q = 0$  (d)  $P = 0, Q = \bar{B}$

1. (d)

$$\bar{Z} = (P + A)(Q + \bar{A})$$

$$\bar{Z} = PQ + AQ + \bar{A}P$$

If

$$Z = \bar{A} + B$$

$$\bar{Z} = \overline{\bar{A} + B} = AB$$

$$Q = \bar{B}, P = 0$$

**Q.2** 24 MHz clock frequency is applied to a cascaded counter of MOD-3, MOD-4 and MOD-5 counters. The lowest output frequency and the overall MOD value of the cascaded counter are

- (a) 600 kHz, 60 (b) 400 kHz, 60  
(c) 400 kHz, 120 (d) 600 kHz, 120


2. (b)

$$\text{Overall MOD} = 3 \times 4 \times 5 = 60$$

Lowest frequency is output frequency

$$f_{\text{out}} = \frac{24 \times 10^6}{60} = 400 \text{ kHz}$$

 **Q.3** For the NMOS logic circuit shown below, if the input  $C = 0$  and  $D = 0$ , then for which combination of  $A$  and  $B$  the output  $Y$  will be 0?



- (a)  $A = 0, B = 1$  (b)  $A = 0, B = 0$   
(c)  $A = 1, B = 1$  (d)  $A = 1, B = 0$

3. (c)

$$Y = \overline{AB + CD}$$

for  $C = D = 0$ ,  $Y = \overline{AB}$   
so,  $Y$  will be 0 when  $A = B = 1$

Q.4 The irredundant minimised logic expression corresponding to the K-map shown below is

YZ \ WX	00	01	11	10
00			1	
01	1	1	1	
11		1	1	1
10		1		

- (a)  $XZ$  (b)  $\overline{W}X\overline{Y} + \overline{W}YZ + W\overline{Y}Z + WXY$   
(c)  $\overline{W}X\overline{Y} + \overline{W}YZ + W\overline{Y}Z + WX\overline{Y}$  (d)  $XZ + \overline{W}YZ + \overline{W}X\overline{Y} + WXY + W\overline{Y}Z$

4. (b)

YZ \ WX	00	01	11	10
00			1	
01	1	1	1	
11		1	1	1
10		1		

$$Z = \overline{W}X\overline{Y} + WXY + \overline{W}YZ + W\overline{Y}Z$$

Q.5 Consider the following statements.

1. A flip-flop can store 1-bit information
2. Race around condition occurs in a level triggered J-K flip-flop when both the inputs are 1
3. Master slave configuration is used in flip-flops to store 2 bits of data
4. A transparent latch consists of a D-type flip-flop

Which of these statements are correct?

- (a) 1 and 2 (b) 1, 3 and 4  
(c) 1, 2 and 4 (d) 2 and 3

5. (c)

Master slave configuration stores 1-bit of data.


Q.6 A certain 8-bit successive approximation type analog to digital converter has full scale voltage of 2.65 V. If the conversion time for  $V_A = 1.5$  V is 75  $\mu$ s, then the conversion time for  $V_A = 2$  V is

- (a) 75  $\mu$ s (b) 25  $\mu$ s  
(c) 225  $\mu$ s (d) 150  $\mu$ s

6. (a)

For successive approximation type of converter, the conversion time is independent of  $V_A$ . Hence, option (a) is correct.

 - Q.7** Assume that the initial value of  $Q$  is 0. After applying the clock signal to the given circuit, the subsequent states of  $Q$  will be



- (a) 0, 1, 0, 1, 0  
(b) 1, 0, 1, 0, 1  
(c) 0, 0, 0, 0, 0  
(d) 1, 1, 1, 1, 1


**7. (b)**

It is a toggle flip-flop, the values toggle

$Q : 0 \rightarrow 1 \rightarrow 0 \rightarrow 1 \rightarrow 0 \rightarrow 1$

↑  
initial state

 - Q.8** The circuit shown below implements a two input NOR gate by using two  $2 \times 1$  multiplexers. The values of  $A$ ,  $B$ , and  $C$  are respectively.



- (a) 0,  $\bar{X}$ , 0  
(b) 1,  $\bar{X}$ , 1  
(c) 0, 0,  $\bar{X}$   
(d) 1, 1,  $X$

**8. (a)**

$$F_0 = XC + Y\bar{C}$$

$$Z = F_1 = B\bar{F}_0 + AF_0$$

for NOR gate,

$$Z = \overline{X+Y} = \bar{X}\bar{Y} = \bar{F}_0B + F_0A$$

for  $A = 0$

$$\bar{F}_0B = \bar{X}\bar{Y}$$

Let us take

$$B = \bar{X} \quad (\text{as only } X \text{ and } \bar{X} \text{ are used in the options})$$

then,

$$\bar{F}_0 = \bar{Y} \Rightarrow F_0 = Y$$

$$F_0 = \bar{C}Y + CX = Y \Rightarrow \text{it is possible for } C = 0$$

so correct combination is  $A = 0, B = \bar{X}, C = 0$

- Q.9** The initial value of output ( $Q_n$ ) of a  $J$ - $K$  flip flop is 0. If it changes to 1 after application of a clock pulse, then the inputs  $K_n$  and  $J_n$  before application of the clock pulse are respectively.
- (a) 0,  $X$  (b)  $X$ , 0  
(c)  $X$ , 1 (d) 1,  $X$

**9. (c)**

Excitation table

$Q_n$	$Q_{n+1}$	$J$	$K$
0	0	0	$X$
0	1	1	$X$
1	0	$X$	1
1	1	$X$	0

- Q.10** The truth table of a combinational circuit is given below

$A$	$B$	$C$	$Z$
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

The Boolean expression for  $Z$  is

- (a)  $(ABC) + (\bar{A}\bar{B}\bar{C})$  (b)  $(\bar{A} + \bar{B} + \bar{C}) + (A + B + C)$   
(c)  $\bar{C} + (A \oplus B)$  (d)  $\bar{C} + (A \odot B)$

**10. (c)**

Using POS form

$$\begin{aligned} Z &= (A + B + \bar{C})(\bar{A} + \bar{B} + \bar{C}) \\ &= (A + B)(\bar{A} + \bar{B}) + \bar{C} \\ &= A \oplus B + \bar{C} \\ &= \bar{C} + (A \oplus B) \end{aligned}$$

**Numerical Answer Type Questions : Q. 11 to Q. 16 carry 1 mark each**

- Q.11** If the number of comparators used in a  $k$ -bit flash type ADC is 15, then the value of  $k$  is \_\_\_\_\_.

**11. (4)**

$$\begin{aligned} \text{Number of comparators} &= 2^k - 1 \\ 2^k - 1 &= 15 \\ 2^k &= 16 \\ k &= 4 \end{aligned}$$

**Q.12** The resolution of a 10-bit analog to digital convertor is \_\_\_\_\_ %.

**12. 0.097 (0.07 to 0.12)**

$$\begin{aligned}\% \text{ Resolution} &= \frac{100}{2^n - 1} = \frac{100}{2^{10} - 1} = \frac{100}{1023} \\ &= 0.097\%\end{aligned}$$

**Q.13**  $(25.5)_8 + (75.4)_8 = (\text{_____})_8$

**13. 123.1 (123 to 123.20)**

$$\begin{aligned}(25.5)_8 + (75.4)_8 &= (123.1)_8 \\ (9)_{10} &= (11)_8 \\ (11)_{10} &= (13)_8 \\ (10)_{10} &= (12)_8\end{aligned}$$

**Q.14** Each cell of a static random memory contains  $n$  - number of MOS transistors. The value of  $n$  is \_\_\_\_\_.

**14. (6)**

**Q.15** If  $(211)_x = (152)_8$ , then the value of  $x$  is \_\_\_\_\_.


**15. (7)**

Converting to decimal equivalent

$$\begin{aligned}(211)_x &= (2x^2 + x + 1)_{10} \\ (152)_8 &= (64 + 40 + 2)_{10} = (106)_{10} \\ 2x^2 + x + 1 &= 106 \\ 2x^2 + x - 105 &= 0 \\ \Rightarrow x &= 7\end{aligned}$$


**Q.16** If  $X$  and  $Y$  logic inputs are available and their respective complements  $\bar{X}$  and  $\bar{Y}$  are not available, then the minimum number of two input NAND gates required to implement  $X \oplus Y$  is \_\_\_\_\_.

**16. (4)**

 

**Multiple Choice Questions : Q.17 to Q.26 carry 2 marks each**

 **Q.17** Consider the combinational logic circuit shown below.



The output  $Q$  can be expressed as

- (a)  $\Sigma m(0, 1, 2, 3, 4, 5, 6)$  (b)  $\Pi M(0)$   
(c)  $\Pi M(0, 1)$  (d)  $\Sigma m(1, 2, 3, 4, 5, 6)$

17. (b)

$S_1$	$S_0$	$C$	$Q$
$\bar{A}$	$\bar{B}$	$C$	$\bar{A}\bar{B}C$
$\bar{A}$	$B$	$1$	$\bar{A}B$
$A$	$\bar{B}$	$1$	$A\bar{B}$
$A$	$B$	$1$	$AB$

$$\begin{aligned} Q &= \bar{A}\bar{B}C + \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + ABC + AB\bar{C} \\ &= \Sigma m(1, 2, 3, 4, 5, 6, 7) \\ &= \Pi M(0) \end{aligned}$$


**Q.18** If the decimal number "4" is coded as "1000" in "4221" BCD system, then what will be the codeword for decimal number "5" in "4221" BCD system?

- (a) 0111 (b) 1001  
(c) 1101 (d) Not possible to say in a unique way

18. (a)

- 4221 code is a self complementing code.  $\therefore 4 + 2 + 2 + 1 = 9$
- For a self complementing code system,  
codeword of "5" = 1's complement of codeword of "4"  $\therefore 5 = 9 - 4$  i.e, 9's complement of 4.  
so, codeword of 5 = 1's complement of (1000)  
= 0111

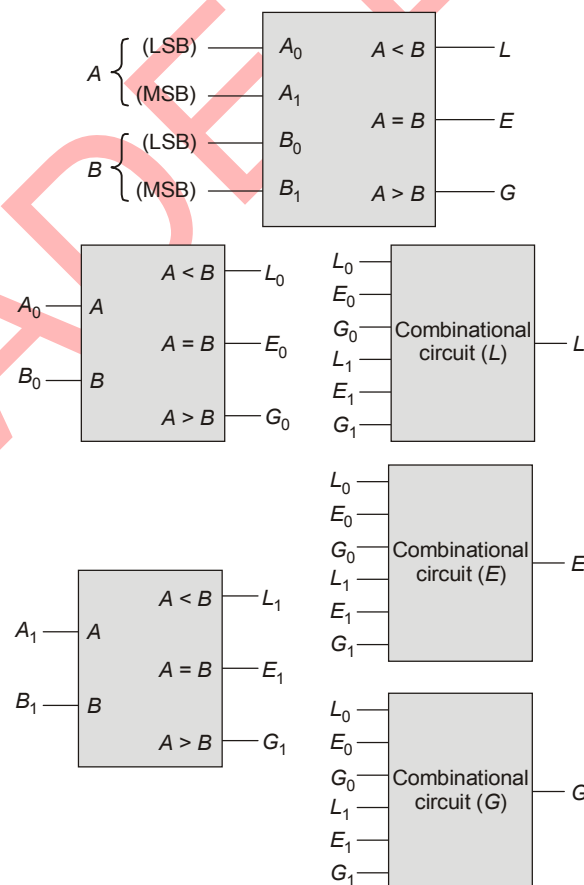
**Q.19** A 2-bit magnitude comparator is designed using two 1-bit magnitude comparators as shown below:



Determine the boolean function for the combinational circuit  $G$ ?

- (a)  $G = E_1G_0 + G_1L_0$  (b)  $G = E_1G_0 + G_1E_0$   
(c)  $G = E_1G_0 + L_1G_0$  (d)  $G = E_1G_0 + G_1$

19. (d)

 


$A > B$  is possible when either of the following conditions is satisfied

1. When  $A_1 > B_1 \Rightarrow$  i.e., when  $G_1 = 1$
2. When  $(A_1 = B_1)$  and  $(A_0 > B_0) \Rightarrow$  i.e., when  $E_1G_0 = 1$

So, the Boolean expression for  $G$  is

$$G = E_1G_0 + G_1$$

 **Q.20** The Boolean expression  $F(X, Y, Z) = \Pi M(0, 2, 4, 7)$  is to be implemented by using a  $4 \times 1$  multiplexer as shown in the figure below. Which one of the following choices of inputs to the multiplexer will realize the required Boolean expression?



- |     | $I_0$ | $I_1$ | $I_2$     | $I_3$     | $S_1$     | $S_0$ |
|-----|-------|-------|-----------|-----------|-----------|-------|
| (a) | 0     | 1     | $X$       | $\bar{X}$ | $Y$       | $Z$   |
| (b) | 0     | 1     | $\bar{X}$ | $X$       | $Y$       | $Z$   |
| (c) | 0     | 1     | $\bar{X}$ | $X$       | $\bar{Y}$ | $Z$   |
| (d) | 1     | 0     | $X$       | $\bar{X}$ | $Y$       | $Z$   |

20. (a)


$X$	$Y$	$Z$	$A$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$YZ \backslash X$	$I_0$	$I_1$	$I_2$	$I_3$
0	0	1	0	1
1	0	1	1	0
	0	1	$X$	$\bar{X}$

Thus solution is option (a).



 **Q.21** Consider the counter circuit and propagation delay table shown below:



Device	Propagation delay
$F_0$	5 $\mu$ sec
$F_1$	4 $\mu$ sec
$F_2$	3 $\mu$ sec
each two-input NAND gate	3 $\mu$ sec

(Assume all the devices are ideal except for some propagation delay).

What is the maximum clock frequency that can be applied to the above counter?

- (a) 125 kHz  
(b) 100 kHz  
(c) 200 kHz  
(d) 142.85 kHz

21. (b)

$T_{\min}$  = minimum clock period required

= time delay from the time of active clock edge to the point of time, where the latest change appears at the input of flip-flops before the application of next active clock edge.

Let us assume active clock edge is applied at  $t = 0$ ,

then,

the latest change in  $Q_0$  appears at  $\Rightarrow t = 5 \mu s$

the latest change in  $Q_1$  appears at  $\Rightarrow t = 4 \mu s$

the latest change in  $Q_2$  appears at  $\Rightarrow t = 3 \mu s$

the latest change in  $D_2$  appears at  $\Rightarrow t = 4 \mu s$


the latest change in  $D_1$  appears at  $\Rightarrow t = 8 \mu s$

the latest change in  $D_0$  appears at  $\Rightarrow t = 10 \mu s$

so  $T_{\min} = 10 \mu\text{sec}$

$$f_{c \max} = \frac{1}{T_{\min}} = \frac{1}{10 \mu \text{sec}} = 100 \text{ kHz}$$

 
**Q.22** Find the minimum number of flip-flops required to design a sequential circuit whose state diagram is given below?



- (a) 2  
(c) 4

- (b) 3  
(d) 5

**22. (a)**

 

the state table for given state diagram:

Present state	Next state		Output	
	for X = 0	for X = 1	for X = 0	for X = 1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	1
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

X = input

state-g and state-e are equal, so we can replace state-g with state-e  
so, simplified state table will be,

Present state	Next state		Output	
	for $X = 0$	for $X = 1$	for $X = 0$	for $X = 1$
$a$	$a$	$b$	0	0
$b$	$c$	$d$	0	0
$c$	$a$	$d$	0	1
$d$	$e$	$f$	0	1
$e$	$a$	$f$	0	1
$f$	$e$	$f$	0	1

now, state- $f$  and state- $d$  are equal. So, we can replace state- $f$  with state- $d$  so, simplified state table will be,

Present state	Next state		Output	
	for $X = 0$	for $X = 1$	for $X = 0$	for $X = 1$
$a$	$a$	$b$	0	0
$b$	$c$	$d$	0	0
$c$	$a$	$d$	0	1
$d$	$e$	$d$	0	1
$e$	$a$	$d$	0	1

now, state-e and state-c are equal. So, we can replace state-e with state-c  
so, simplified state table will be,

Present state	Next state		Output	
	for $X = 0$	for $X = 1$	for $X = 0$	for $X = 1$
$a$	$a$	$b$	0	0
$b$	$c$	$d$	0	0
$c$	$a$	$d$	0	1
$d$	$c$	$d$	0	1

- it is not possible to reduce the state table further, as there are no more equal states.
- so, minimum number of states required to design the circuit = 4.  
and minimum number of flip-flops required = 2.

**Q.23** An 8-bit digital ramp ADC with a 40 mV resolution uses a clock frequency of 2.5 MHz and a comparator with threshold voltage  $V_T = 1$  mV. The digital output for  $V_A = 6$  V is

- (a) 10010111      (b) 10010110  
(c) 10111110      (d) 10111111


23. (a)

$$\begin{aligned} (\text{Digital Equivalent})_{10} \times \text{Resolution} &> V_A + V_T \\ &> 6000 \text{ mV} + 1 \text{ mV} \\ (\text{Digital Equivalent})_{10} \times 40 \text{ mV} &> 6001 \text{ mV} \end{aligned}$$

$$(\text{Digital Equivalent})_{10} > \frac{6001}{40} = 150.025 \Rightarrow 151 \text{ is the next quantization level}$$

so,                    digital output =  $(10010111)_2 \Rightarrow (151)_{10}$

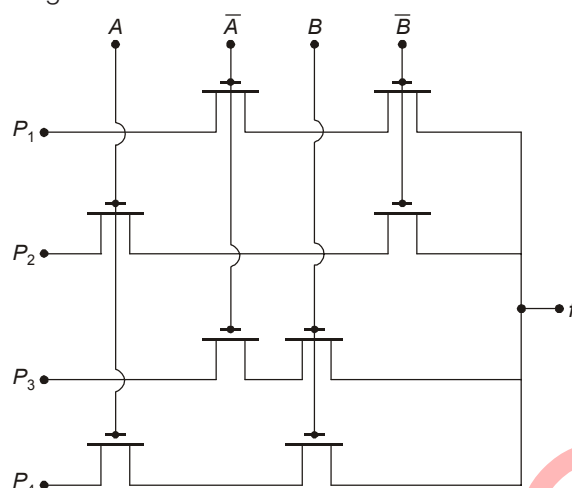**Q.24** Consider an NMOS pass logic network shown below:



if  $A, B$  are input variables and  $f$  is output variable, then for which combination of  $P_1, P_2, P_3$  and  $P_4$  the circuit will behave as EX-OR gate?


- (a)  $P_1 = P_4 = 1, P_2 = P_3 = 0$
- (b)  $P_1 = P_4 = 0, P_2 = P_3 = 1$
- (c)  $P_1 = P_3 = 1, P_2 = P_4 = 0$
- (d)  $P_1 = P_3 = 0, P_2 = P_4 = 1$

**24. (b)**


$A$	$B$	$f$
0	0	$P_1$
0	1	$P_2$
1	0	$P_3$
1	1	$P_4$


so, the given pass logic network acts as EX-OR gate when  $P_1 = P_4 = 0$  and  $P_2 = P_3 = 1$ .

 **Q.25** The state transition diagram for the logic circuit is shown below



The logic circuit will be

 

 

25. (b)

from the state diagram,

When  $A = 1 \Rightarrow Q_{n+1} = Q_n \Rightarrow$  next state is same as present state.

When  $A = 0 \Rightarrow Q_{n+1} = \bar{Q}_n \Rightarrow$  next state is the toggle of present state.

In (a) and (c) case, when input  $A = 1$  and  $Q = 1$ , they toggle,


Hence, correct representation in option (b).

**Q.26** A half adder is implement with XOR and AND gates. A full adder is implemented with two half adders and one OR gate. The propagation delay of an XOR gate is twice that of an AND/OR gate. The propagation delay of an AND/OR gate is  $1.2 \mu\text{sec}$ . A 4-bit ripple carry binary adder is implemented by using full adders. The total propagation delay of this 4-bit binary adder is

- (a)  $19 \mu\text{sec}$  (b)  $19.2 \mu\text{sec}$   
(c)  $38 \mu\text{sec}$  (d)  $38.4 \mu\text{sec}$

26. (b)

For one full Adder :

 


for one FA,

delay to produce sum  $\Rightarrow t_{ds} = 4.8 \mu\text{s}$

delay to produce carry  $\Rightarrow t_{dc} = 4.8 \mu\text{s}$


for 4-bit ripple carry adder :

 

$$t_d = 3t_{dc} + t_{ds} = 4(4.8) \mu\text{s} = 19.2 \mu\text{s}$$

**Numerical Answer Type Questions : Q.27 to Q.33 carry 2 marks each**

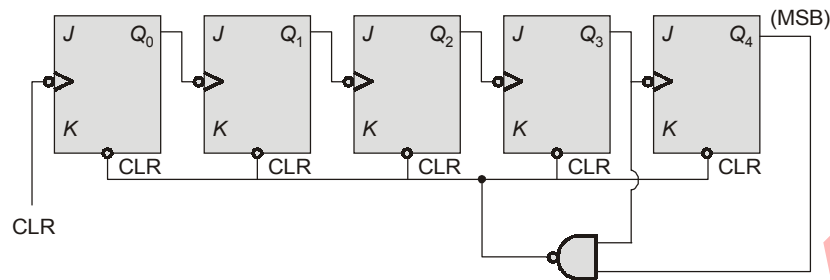**Q.27** The MOD-number of the asynchronous counter shown in the figure below is



**27. (24)**

When  $Q_4Q_3$  is 11, then  $CLR = 0$ , hence the count goes back to 00000.

$$\begin{array}{ccccccc} Q_4 & Q_3 & Q_2 & Q_1 & Q_0 & & Q_4 & Q_3 & Q_2 & Q_1 & Q_0 & & Q_4 & Q_3 & Q_2 & Q_1 & Q_0 \\ 0 & 0 & 0 & 0 & 0 & \longrightarrow & 1 & 0 & 1 & 1 & 1 & \longrightarrow & 0 & 0 & 0 & 0 & 0 \end{array}$$

Thus, counter counts 0 - 23, and clears at 24. It's a MOD-24 counter.


**Q.28** If the maximum frequency with which a 4-bit binary ripple counter can work is 25 MHz, then the propagation delay from CLK to Q of each flip-flop is \_\_\_\_\_ nsec.

**28. (10)**

$$f_{\max} = \frac{1}{nt_{pd}} ; \quad t_{pd} = \text{propagation delay of each flip-flop and } n = \text{number of flip flops}$$

$$\begin{aligned} t_{pd} &= \frac{1}{n \times 25 \times 10^6} \text{ sec} \\ &= \frac{1000}{4 \times 25} \times 10^{-9} \text{ sec} = 10 \text{ nsec} \end{aligned}$$

**Q.29**

 


Consider the circuit shown above. If the input clock frequency is 1 kHz, then the dynamic average power dissipated by the CMOS inverter circuit is \_\_\_\_\_ mW.

**29. 12.5 (12.4 to 12.6)**

$$\text{The input frequency of CMOS inverter} = f_{\text{in}} = \frac{f_{\text{clk}}}{8} = \frac{1 \times 10^3}{8} \text{ Hz}$$

$$\begin{aligned} P_{\text{dissipation}} &= CV_{DD}^2 f_{\text{in}} \\ &= 4 \times 10^{-6} \times 25 \times \frac{1 \times 10^3}{8} \text{ W} \\ &= \frac{100}{8} \text{ mW} = 12.5 \text{ mW} \end{aligned}$$

 **Q.30** The initial state ( $Q_1 Q_0$ ) of the counter shown below is (00). The minimum number of clock pulses required after which the state ( $Q_1 Q_0$ ) goes to (00) again is \_\_\_\_\_.




30. (4)

Clk No.	$Q_1$	$Q_2$	
0	0	0	→ initial
1	1	0	
2	1	1	
3	0	1	
4	0	0	

It's a Johnson counter after 4 clock pulses the state ( $Q_1 Q_0$ ) will be (00) again.

 **Q.31** The initial contents of a 4-bit serial-in-parallel out, right shift, shift register is shown in the given figure is 0110. By the end of 7<sup>th</sup> clock pulse from initial state, the number of times the LED will be in ON state is \_\_\_\_\_.

(Assume logic 1 as +5 V and logic 0 as -5 V)



31. (3)

Clk No.	$D_{in}$ before clk pulse	$Q_3$	$Q_2$	$Q_1$	$Q_0$	Z after clk pulse	LED state
0	-	0	1	1	0	1	OFF
1	1	1	0	1	1	0	ON
2	0	0	1	0	1	1	OFF
3	1	1	0	1	0	1	OFF
4	1	1	1	0	1	1	OFF
5	1	1	1	1	0	1	OFF
6	1	1	1	1	1	0	ON
7	0	0	1	1	1	0	ON

**Q.32** An  $n$ -bit A/D convertor is required to convert an analog input in the range 0 - 5 V with a maximum error of 10 mV on each conversion. The minimum value of  $n$  is \_\_\_\_\_.

32. (9)

$$\text{maximum quantization error} = \Delta = \frac{5 \text{ V}}{(2^n - 1)}$$

$$\text{so, } \frac{5 \text{ V}}{(2^n - 1)} \leq 10 \text{ mV}$$


$$(2^n - 1) \geq 500$$

$$2^n \geq 501$$

$$n \geq 9$$

$$n_{\min} = 9$$

 **Q.33** Consider the 4-bit DAC shown in the following figure. The output voltage  $V_0$  for an input data 0110 will be \_\_\_\_\_ V.



33. 3.75 (3.60 to 3.80)

$$V_0 = -R V_{\text{ref}} \left[ \frac{b_3}{2R} + \frac{b_2}{4R} + \frac{b_1}{8R} + \frac{b_0}{16R} \right]$$

$$= -\frac{V_{\text{ref}}}{16} [8b_3 + 4b_2 + 2b_1 + b_0]$$

$$V_0 = -\frac{V_{\text{ref}}}{16} [\text{decimal equivalent of input binary code}]$$

$$\text{given input binary code} = (0110)_2 = (6)_{10}$$

$$\text{so, } V_0 = \frac{10}{16}(6) = 3.75 \text{ V}$$

○○○○