



MADE EASY

India's Best Institute for IES, GATE & PSUs

Corporate Office (Delhi): 44-A/1 Kalu Sarai (Sarvapriya Vihar), New Delhi-16, **Ph:** 011-45124612, 9958995830

Visit us at: www.madeeasy.in | **E-mail us at:** info@madeeasy.in

Delhi | Hyderabad | Noida | Bhopal | Jaipur | Lucknow | Indore | Pune | Bhubaneswar | Kolkata | Patna

Open Lockdown Period Practice Series for GATE (Also useful for ESE & Other Exams)

EE : ELECTRICAL ENGINEERING

TEST No. - 01 | ELECTRIC CIRCUITS

Read the following instructions carefully


1. This question paper contains 33 MCQ's & NAQ's. Bifurcation of the questions are given below:

Subjectwise Test Pattern					
Questions	Question Type	No. of Questions	Marks	Total Marks	Negative Marking
1 to 9	Multiple Choice Ques.	9	1	9	0.33
10 to 16	Numerical Answer Type Ques.	7	1	7	None
17 to 25	Multiple Choice Ques.	9	2	18	0.66
26 to 33	Numerical Answer Type Ques.	8	2	16	None
Total Questions : 33		Total Marks : 50		Total Duration : 90 min	

2. Choose the closest numerical answer among the choices given.

Multiple Choice Questions : Q.1 to Q.9 carry 1 mark each

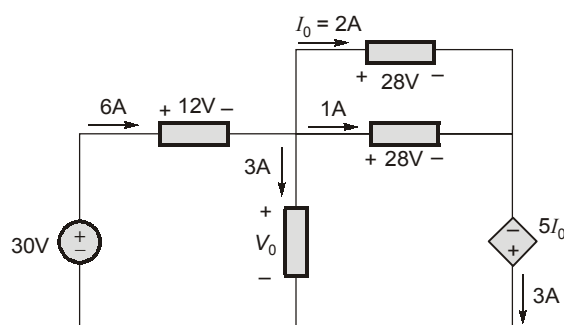Q.1 The voltage V_0 in the circuit shown below is,



- (a) 20 V (b) 22 V
(c) 18 V (d) 19 V

1. (c)

Since total power absorbed or delivered in the circuit

$$\Rightarrow \Sigma P = 0;$$


then $-30 \times 6 + 6 \times 12 + 3 V_0 + 28 + 28 \times 2 - 3 \times 10 = 0$

$$72 + 84 + 3 V_0 = 210;$$

or $3 V_0 = 54$

$$\Rightarrow V_0 = 18 \text{ V}$$

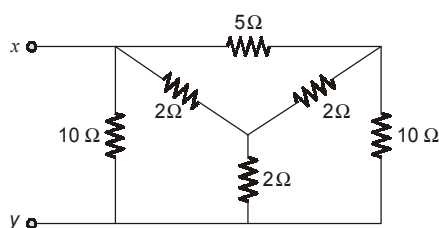
Q.2 The equivalent resistance between terminals x-y in the resistive network is




- (a) $1.048\ \Omega$ (b) $2.105\ \Omega$
(c) $3.045\ \Omega$ (d) $2.375\ \Omega$

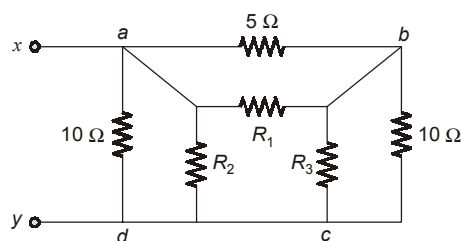2. (d)

Converting Y circuit to Δ circuit, the circuit is as shown below,



Further simplifying the circuit we get,

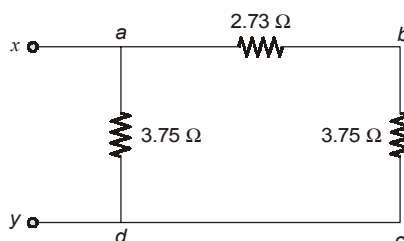

$$R_1 = 2 + 2 + \frac{2 \times 2}{2 + 0} = 6 \, \Omega$$

Due to symmetry of the network inside star network,

$$R_1 = R_2 = R_3 = 6 \, \Omega$$


$$R_{ab} = \frac{5R_1}{5 + R_1} = 2.73 \, \Omega$$

$$R_{bc} = \frac{10R_3}{10 + R_3} = 3.75 \, \Omega$$

$$R_{ad} = \frac{10R_2}{10 + R_2} = 3.75 \, \Omega$$

$$R_{x-y} = R_{ad} \parallel (R_{ab} + R_{bc}) = 2.375 \, \Omega$$

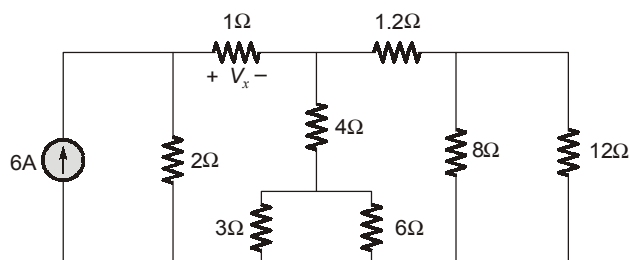
Q.3 In the circuit shown below the value of voltage V_x is




- (a) 1 V (b) 2 V
(c) 3 V (d) 4 V

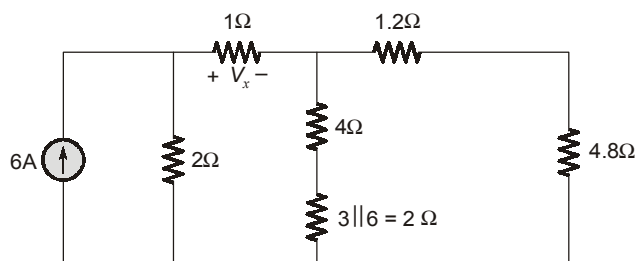3. (b)

The given circuit can be reduced to below ckt.



Further it can be reduced as ;

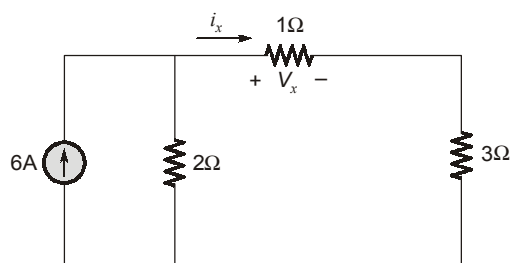

Now applying current division, we get


$$i_x = \frac{2}{2+1+3} \times 6 = 2A;$$

$$V_x = 1 \times 2 = 2V$$

Q.4 A symmetrical T-section has the following impedances at terminal 1 1'.

$$Z_{OC} = 800 \Omega$$

$$Z_{SC} = 600 \Omega$$

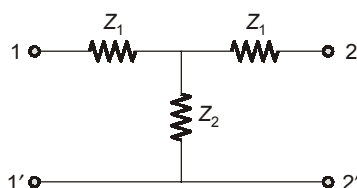

The parameters Z_1, Z_2 of the network are:

- (a) $400 \Omega, 800 \Omega$ (b) $800 \Omega, 800 \Omega$
(c) $400 \Omega, 600 \Omega$ (d) $400 \Omega, 400 \Omega$

4. (d)

$$Z_1 + Z_2 = 800, \text{ O.C condition}$$

$$Z_1 + \frac{Z_1 Z_2}{Z_1 + Z_2} = 600, \text{ S.C. condition}$$

$$Z_1 + \frac{Z_1(800 - Z_1)}{800} = 600$$


$$Z_1^2 = 1600 Z_1 + 48 \times 10^4 = 0$$

$$(Z_1 - 800)^2 = (\pm 400)^2$$

$$Z_1 = 400 \Omega \text{ or } 1200 \Omega$$

If $Z_1 = 1200 \Omega$ then $Z_2 = -400 \Omega$ (not possible)
therefore, $Z_1 = 400 \Omega, Z_2 = 400 \Omega$

Q.5 In the circuit shown below

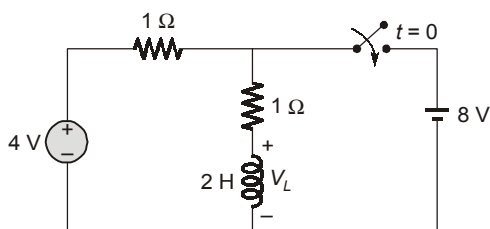

the switch is opened for a long time and it is closed at $t = 0$. The energy stored by the inductor at steady state is

- (a) 50 J (b) 100 J
(c) 64 J (d) 54 J


5. (c)

at $t = \infty$, the circuit behaves as shown below


$$i_L(\infty) = \frac{8}{1} = 8 \text{ A}$$

$$\text{Energy stored} = \frac{1}{2} L I^2$$
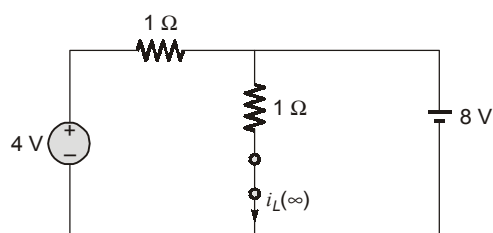
$$\Rightarrow \frac{1}{2} (2)(8)^2 = 64 \text{ J}$$



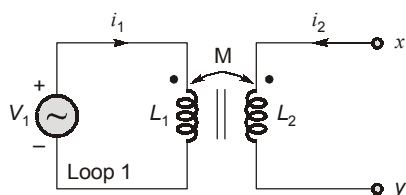Q.6 In the circuit shown below, the open circuit voltage (V_{xy}) in term of M , is



- (a) $M \frac{V_1}{L_1}$ (b) $M \frac{V_2}{L_2}$
(c) $M \frac{V_1}{L_2}$ (d) $M \frac{V_2}{L_1}$

6. (a)

Applying KVL,

$$V_{xy} - j\omega L_2 i_2 - j\omega M i_1 = 0$$

as $i_2 = 0$

then, $V_{xy} - j\omega M i_1 = 0$... (i)

applying KVL in loop 1


$$V_1 = j\omega L_1 i_1$$

... (ii)

Using value of i_1 from equation (ii) in equation (i)

$$V_{xy} = j\omega M \left[\frac{V_1}{j\omega L_1} \right] = \frac{MV_1}{L_1}$$

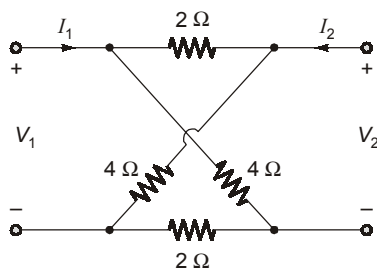Q.7 In the circuit shown below, open circuit parameters Z_{11} and Z_{21} are respectively,




- (a) 3Ω and 1Ω (b) 4Ω and 2Ω
(c) 3Ω and 4Ω (d) 2Ω and 1Ω

7. (a)

For Z_{11} and Z_{21}

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}, \quad Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

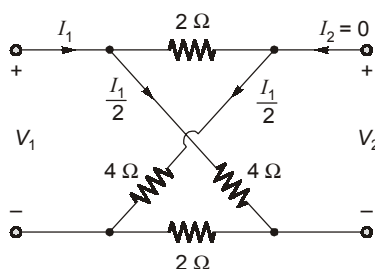From the circuit as shown below, we can get



Output port O.C,

$$Z_{11} = \frac{V_1}{I_1} = 6 \parallel 6 = 3 \Omega$$


$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0},$$

Using KVL, we can get

$$-V_2 + \frac{4I_1}{2} - 2\frac{I_1}{2} = 0; \quad \Rightarrow \quad V_2 = I_1$$

then $\frac{V_2}{I_1} = Z_{21} = 1 \Omega$

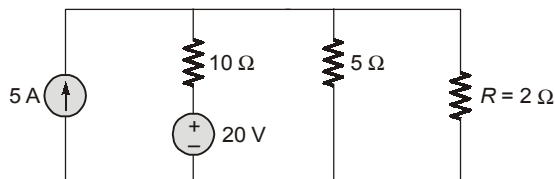Q.8 The current flowing through resistor ' R ' in the circuit shown below is



(a) 4.38 A


(b) 10 A

(c) 5.38 A

(d) 3.38 A

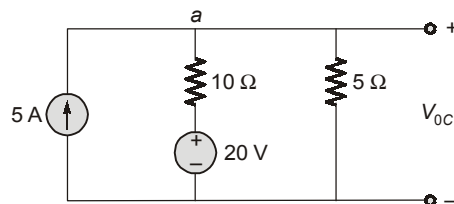
8. (a)

Let R be removed, the circuit is shown as below



Now applying KCL at node a ,
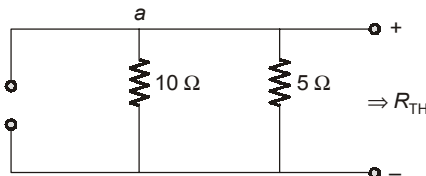
$$\begin{aligned} \frac{V_{oc}}{5} + \frac{V_{oc} - 20}{10} &= 5 \\ 0.2 V_{oc} + 0.1 V_{oc} - 2 &= 5 \\ V_{oc} &= 23.33 \text{ V} \end{aligned}$$




Now equivalent thevenin's resistance,

$$\begin{aligned} R_{Th} &= \frac{10 \times 5}{10 + 5} \\ R_{Th} &= 3.33 \Omega \end{aligned}$$

Current through $R = 2 \Omega$ resistor,

$$\begin{aligned} I_{2\Omega} &= \frac{V_{oc}}{R_{Th} + R} = \frac{23.33}{3.33 + 2} \\ I_{2\Omega} &= 4.38 \text{ A} \end{aligned}$$

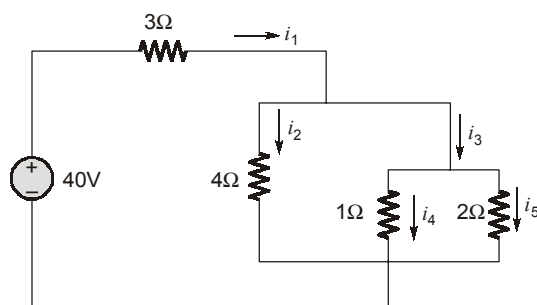- Q.9** For the circuit shown below, the current i_3 is
 (a) 7.2 A (b) 8.3 A
 (c) 9.6 A (d) 10.2 A



9. (c)

The total equivalent resistance of the circuit ;

$$R_{eq} = 3 + (2 \parallel 4 \parallel 1) = 3 + 0.5714 = 3.5714 \Omega$$

Now;


$$i_1 = \frac{40}{3.5714} = 11.2 A$$

$$\therefore i_3 = \frac{4}{\left(4 + \frac{2}{3}\right)} \times i_1 = \frac{4}{4.667} \times 11.2$$

$$i_3 = 9.6 A$$

Numerical Answer Type Questions : Q. 10 to Q. 16 carry 1 mark each

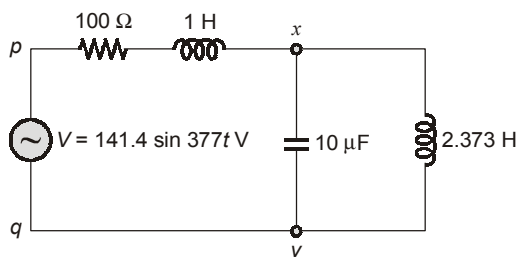- Q.10** The total power dissipated in the circuit shown below is _____ W.



10. 100 (99.00 to 101.00)

The net impedance between x-y terminals

$$Z_{xy} = \frac{(j\omega L) \left(\frac{1}{j\omega C} \right)}{j\omega L + \frac{1}{j\omega C}} = \frac{\frac{L}{C}}{j \left(\omega L - \frac{1}{\omega C} \right)}$$


$$= \frac{\frac{2.373}{10 \times 10^{-6}}}{j \left(377 \times 2.373 - \frac{1}{377 \times 10 \times 10^{-6}} \right)} = -j377 \Omega$$

$$\text{Total impedance} = -j377 + 100 + j377 = 100 \Omega$$

$$I = \frac{141.4}{\sqrt{2} \times 100} = 1 A$$

$$\text{Power dissipated} = I^2 R = 1^2 \times 100 = 100 W$$

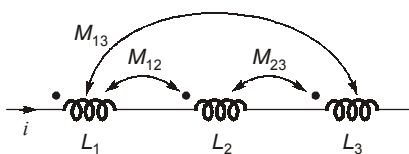Q.11 The total inductance of the three series connected coupled coils is _____ H.



Given:

$$\begin{array}{lll} L_1 = 1 \text{ H} & L_2 = 2 \text{ H} & L_3 = 5 \text{ H} \\ M_{12} = 0.5 \text{ H} & M_{23} = 1 \text{ H} & M_{13} = 1 \text{ H} \end{array}$$

11. 13 (12.50 to 13.50)

For coil 1 :

$$\begin{aligned} L_1 + M_{12} + M_{13} &= 1 + 0.5 + 1 \\ &= 2.5 \text{ H} \end{aligned}$$


$$\text{For coil 2: } L_2 + M_{23} + M_{12} = 2 + 1 + 0.5 = 3.5 \text{ H}$$

$$\text{For coil 3: } L_3 + M_{13} + M_{23} = 5 + 1 + 1 = 7 \text{ H}$$

Net Inductance,

$$\begin{aligned} \Rightarrow L_1 + M_{12} + M_{13} + L_2 + M_{23} + M_{12} + L_3 + M_{13} + M_{23} \\ 2.5 + 3.5 + 7 = 13 \text{ H} \end{aligned}$$

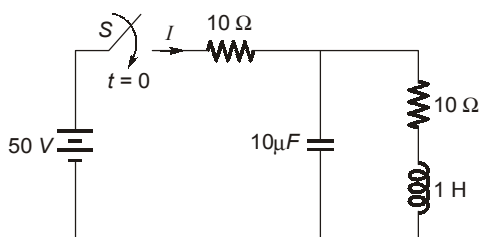Q.12 The network shown below was at rest initially. The value of initial current I when switch S is closed at $t = 0$ is _____ A.




12. 5.00 (4.90 to 5.10)

At

$$t = 0^+$$

$$v_C(0^-) = v_C(0^+) = 0 \Rightarrow \text{short circuited}$$
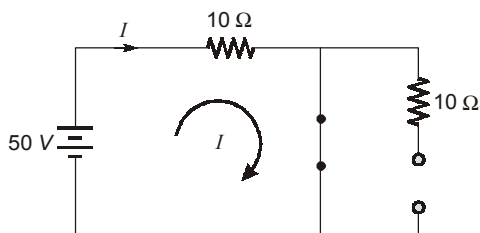
$$i_L(0^-) = i_L(0^+) = 0 \Rightarrow \text{open circuited}$$



Applying KVL

$$\begin{aligned} 10I &= 50 \\ I &= 5 \text{ A} \end{aligned}$$

Q.13 A 220 V, 100 Hz ac source supplies a series RLC circuit with a capacitor and a coil. If the coil has $50 \text{ m}\Omega$ resistance and 5 mH inductance, then at resonance at $f = 100 \text{ Hz}$, the lower half power frequency is _____ Hz.

13. 99.20 (99.00 to 100.00)

Resonant frequency, $f_0 = \frac{1}{2\pi\sqrt{LC}}$

$$100 = \frac{1}{2\pi\sqrt{5 \times 10^{-3} \times C}}$$


$$C = \frac{1}{4\pi^2 \times 100^2 \times 5 \times 10^{-3}} = 507 \mu\text{F}$$

$$Q = \frac{\omega_0^2}{R} = \frac{2\pi \times 100 \times 5 \times 10^{-3}}{50 \times 10^{-3}} = 62.83$$


$$\text{Bandwidth} = \frac{f_0}{Q} = \frac{100}{62.83} = 1.59 \text{ Hz}$$

$$\begin{aligned} \text{lower half power frequency} &= f_0 - \frac{\text{B.W.}}{2} \\ &= 100 - \frac{1.59}{2} = 99.205 \text{ Hz} \end{aligned}$$

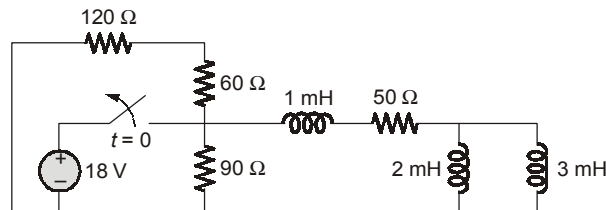Q.14 The time constant of the circuit is _____ μsec .



14. 20 (19.00 to 21.00)

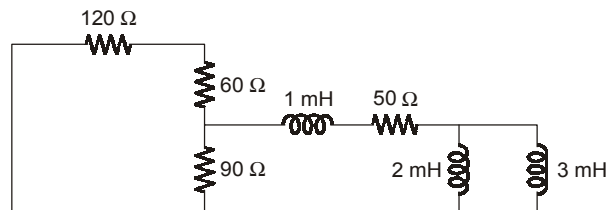


From the above circuit, we can get,

$$L_{eq} = \frac{2 \times 3}{2 + 3} + 1 = 2.2 \text{ mH}$$

$$R_{eq} = \frac{90(60 + 120)}{90 + 180} + 50 = 110 \Omega$$


Time constant, $\tau = \frac{L_{eq}}{R_{eq}} = \frac{2.2 \times 10^{-3}}{110} = 20 \mu\text{sec}$

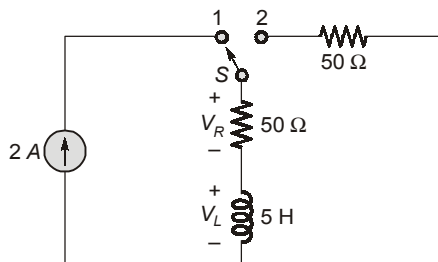- Q.15** In the circuit shown below switch S is kept at position 1 for a long time. Then at $t = 0$ the switch is transferred to position 2. The voltage (magnitude) across inductor at $t = 0^+$ is _____ (in Volts).




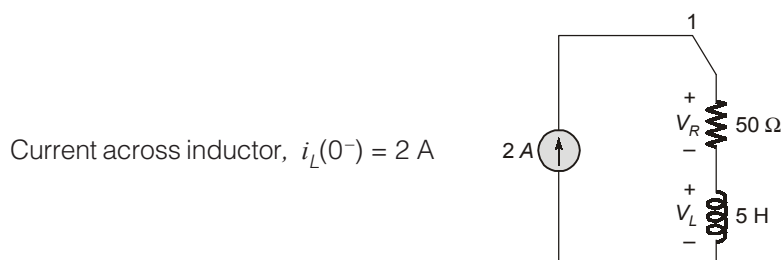- 15. 200 (198.00 to 202.00)**

At $t = 0^-$, the circuit behaves as shown below



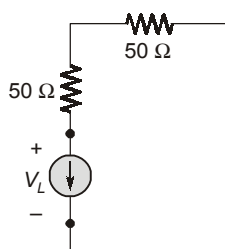
Now at $t = 0^+$, the circuit behaves as shown below



Now applying KVL in the circuit, we get,

$$\begin{aligned} V_L + 50(2) + 50(2) &= 0 \\ V_L &= -200 \text{ Volts} \\ |V_L| &= 200 \text{ Volts} \end{aligned}$$

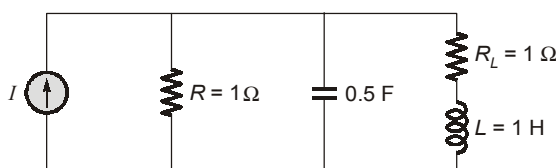- Q.16** In the circuit shown below, the value of admittance at resonant frequency is _____ Ω .



- 16. 1.50 (1.40 to 1.60)**

The circuit admittance seen by the current source is

$$\begin{aligned} Y &= \frac{1}{R} + j\omega C + \frac{1}{R_L + j\omega L} \\ &= \frac{1}{R} + j\omega C + \frac{R_L - j\omega L}{R_L^2 + \omega^2 L^2} \\ &= \frac{1}{R} + \frac{R_L}{R_L^2 + \omega^2 L^2} + j\left(\omega C - \frac{\omega L}{R_L^2 + \omega^2 L^2}\right) \end{aligned}$$

at resonance, imaginary part of Y must be zero

$$\omega_0 C = \frac{\omega_0 L}{R_L^2 + \omega_0^2 L^2}$$

$$R_L^2 + \omega_0^2 L^2 = \frac{L}{C}$$

$$\omega_0 = \left[\frac{1}{LC} - \frac{R_L^2}{L^2} \right]^{1/2}$$

Substituting value of L, R, C

$$\omega_0 = \left[\frac{1}{1 \times 0.5} - \frac{1^2}{1^2} \right]^{1/2} = 1 \text{ rad/sec}$$


admittance at resonance is,

$$Y = \frac{1}{R} + \frac{R_L}{R_L^2 + \omega_0^2 L^2}$$

$$= 1 + \frac{1}{1 + 1^2 \cdot 1^2} = 1.5 \text{ } \Omega$$

Multiple Choice Questions : Q.17 to Q.25 carry 2 marks each

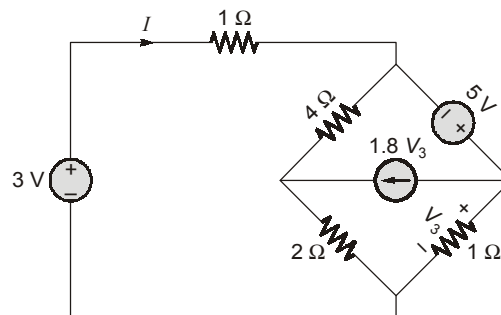Q.17 Find I and V_3 in the circuit given below




- (a) 4.37 A, 2.62 V
 (c) 5.37 A, 3.62 V

- (b) 5.37 A, 2.62 V
 (d) 4.37 A, 3.62 V

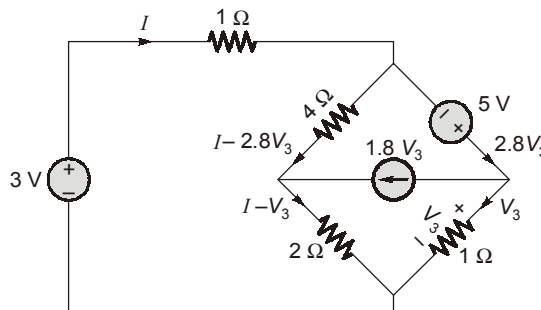17. (c)

Showing the corresponding currents in all the branches, the circuit is shown as below



Now we apply KVL in outer loop

$$-3 + I(1) - 5 + V_3 = 0$$

$$I + V_3 = 8$$

Applying KVL in bridge,

...(i)

Current through inductive branch,

$$I_L = \frac{10\angle 0^\circ}{1 + j0.314} = \frac{10\angle 0^\circ}{1.048\angle 17.34^\circ}$$

$$I_L = 9.54\angle -17.43^\circ \text{ A}$$

Complex power absorbed by inductive circuit,


$$\begin{aligned} S &= VI_L^* \\ &= 10\angle 0^\circ \times 9.54\angle 17.43^\circ \\ &= 95.4\angle 17.43^\circ \text{ VA} \\ S &= 91.01 + j28.57 \text{ VA} \end{aligned}$$

$$X_C = \frac{V_C^2}{Q_C} = \frac{20^2}{10} = 40\Omega$$

$$C = \frac{1}{2\pi \times 50 \times 40}$$

$$C = 79.57 \mu\text{F}$$

Q.20 For the circuit shown below, what value of α will produce $\left| \frac{V_0}{V_s} \right| = 10$, for $R_1 = R_2 = R_3 = R_4$.

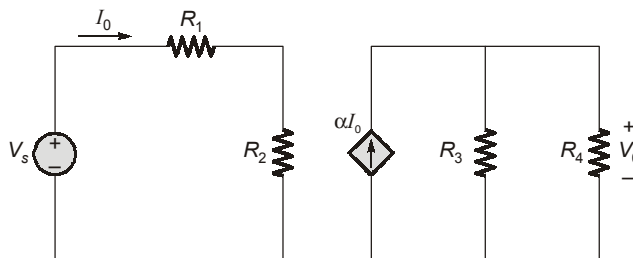

- (a) 10 (b) 20
(c) 30 (d) 40

20. (d)

From the given circuit;

$$I_0 = \frac{V_s}{R_1 + R_2}; \text{ \& } V_0 = \alpha I_0 \times (R_3 \parallel R_4)$$

$$V_0 = \frac{\alpha V_s}{R_1 + R_2} \times \frac{R_3 R_4}{R_3 + R_4}$$


$$\frac{V_0}{V_s} = \frac{\alpha(R_3 R_4)}{(R_1 + R_2)(R_3 + R_4)}$$

For $R_1 = R_2 = R_3 = R_4$;

$$\left| \frac{V_0}{V_s} \right| = \frac{\alpha}{2R} \times \frac{R}{2} = \frac{\alpha}{4} = 10$$

$$\Rightarrow \alpha = 40$$

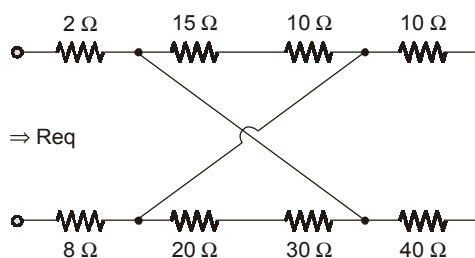
Q.21 The equivalent resistance R_{eq} for the following circuit is,



- (a) 20.5Ω (b) 24.5Ω
(c) 22.5Ω (d) 18.5Ω

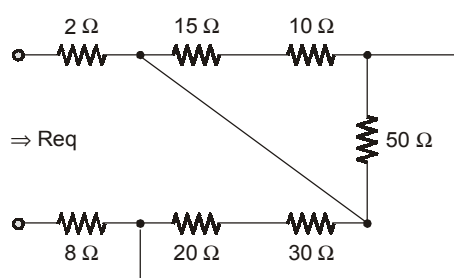
21. (c)

1st combine 10Ω and 40Ω resistors and redrawing the circuit.




We now have,
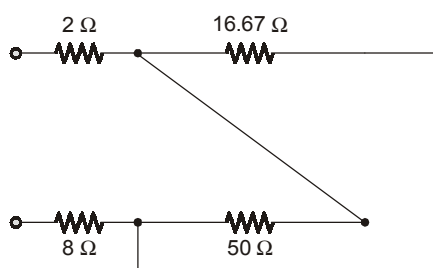
$$(10 \Omega + 15 \Omega) \parallel 50 \Omega = 16.67 \Omega$$



$$\begin{aligned} \text{equivalent resistance} &= 2 \Omega + (50 \Omega \parallel 16.67 \Omega) + 8 \Omega \\ &= 22.5 \Omega \end{aligned}$$

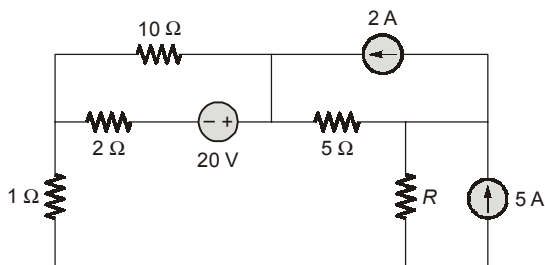
Q.22 The maximum power transferred to resistor R in the circuit shown below is



- (a) 66 W (b) 55 W
(c) 45 W (d) 60 W

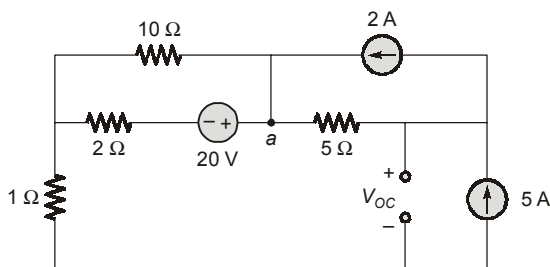22. (a)

First R is removed and circuit behaves as shown below,



Current through 1Ω resistor = 5 A (downwards)

Hence, $V_{1\Omega} = 5\text{ V}$

At node a , assuming node voltage V volts, applying KCL,

$$\frac{V-5}{10} + \frac{V-20-5}{2} + \frac{V-V_{oc}}{5} = 2$$

$$0.1V - 0.1(5) + 0.5V - 10 - 0.5(5) + 0.2V - 0.2V_{oc} = 2$$

$$0.8V - 0.6(5) = 12 + 0.2V_{oc}$$

$$0.8V - 0.2V_{oc} = 12 + 3 = 15 \quad \dots(i)$$


at node 6 , nodal analysis

$$\frac{V_{oc} - V}{5} + 2 = 5$$

$$0.2V_{oc} - 0.2V = 3 \quad \dots(ii)$$

Solving equation (i) and (2)

$$V_{oc} = 45\text{ V}$$

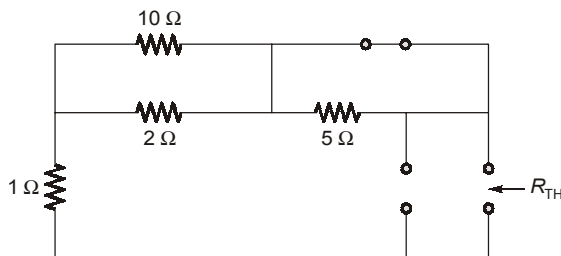


$$R_{Th} = \{(10 \parallel 2) + 1\} + 5$$

$$= \left(\frac{20}{12} + 1\right) + 5 = 7.67\Omega$$

$$P_{max} = \frac{V_{oc}^2}{4R} = \frac{45^2}{4 \times 7.67} = 66\text{ W}$$

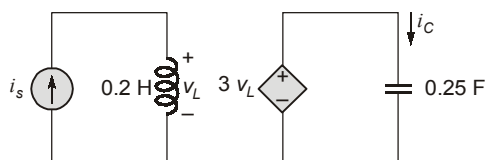Q.23 In the circuit of figure, $i_s(t) = 4 \sin 4t\text{ A}$. The $i_c(t)$ will be



(a) $4.6 \sin 4t\text{ A}$

(b) $-4.8 \sin 4t\text{ A}$

(c) $9.8 \sin 4t\text{ A}$

(d) $-9.6 \sin 4t\text{ A}$

23. (d)

The voltage across inductor is,

$$V_L = L \frac{di_L}{dt} = L \frac{di_s(t)}{dt}$$


Current across capacitor is given by,

$$i_c = C \frac{dv_c}{dt}$$

$$V_c = 3V_L$$

$$\Rightarrow i_c = 3C \frac{dV_L}{dt} = 3C.L \frac{d^2 i_s(t)}{dt^2} = -9.6 \sin 4t \text{ A}$$

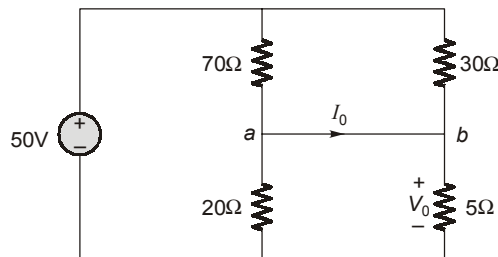Q.24 The voltage V_0 and current I_0 in the given circuit are ;



(a) 8 V, 0.2 A


(b) 10 V, 0.2 A

(c) 8 V, 0.3 A

(d) 10 V, 0.3 A

24. (a)

∴ From the circuit;

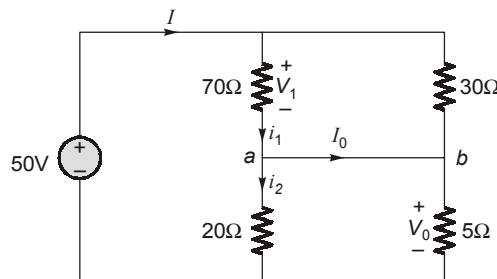

We can get ;

$$I = \frac{50}{(70 \parallel 30) + (20 \parallel 5)} = \frac{50}{(21 + 4)} = 2A$$

∴

$$V_1 = 21 \times I = 42 \text{ V, \& } V_0 = 4I = 8V$$

$$i_1 = \frac{V_1}{70} = 0.6 \text{ A; } i_2 = \frac{V_0}{20} = 0.4 \text{ A}$$

Now, KCL at node 'a',

$$i_1 = i_2 + I_0 ; I_0 = 0.6 - 0.4 = 0.2 \text{ A}$$

Hence,

$$V_0 = 8 \text{ V, } I_0 = 0.2 \text{ A}$$

Q.25 A dc voltage of 100 V is applied to a coil having $R = 10 \Omega$, $L = 10 \text{ H}$, the value of current 0.1 sec after the switching on and the time taken by the current to reach half of its final value are respectively,

(a) 0.95 A, 0.69 sec

(b) 0.95 A, 0.49 sec

(c) 0.85 A, 0.69 sec

(d) 0.85 A, 0.49 sec

25. (a)

$$\text{Final current } I = \frac{V}{R} = \frac{100}{10} = 10 \text{ A}$$

$$T(\text{time constant}) = \frac{L}{R} = \frac{10}{10} = 1 \text{ sec}$$

The changing current is given by

$$i = I(1 - e^{-t/\tau})$$

or

$$i = 10(1 - e^{-t})$$

Value of current 0.1 sec later is

$$i = 10(1 - e^{-0.1}) = 0.95 \text{ A}$$

Current half of final value will be


$$5 = 10(1 - e^{-t})$$

$$0.5 = (1 - e^{-t})$$

$$t = 0.69 \text{ sec}$$

Numerical Answer Type Questions : Q. 26 to Q. 33 carry 2 marks each

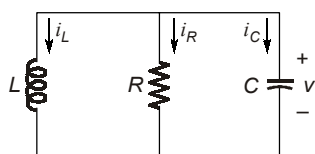Q.26 In the circuit shown in figure, $L = 1 \text{ mH}$ and $C = 100 \mu\text{F}$, choose $R = 0.1 R_C$. Where R_C is the value required to achieve critical damping, $R = \underline{\hspace{2cm}} \times 10^{-3} \Omega$



26. 158.10 (157.50 to 158.50)

For critical damping, $L = 1 \text{ mH}$, $C = 100 \mu\text{F}$ choose $\xi = 1$

and

$$\xi = \frac{1}{2R_C} \sqrt{\frac{L}{C}} = 1$$

$$R_C = \frac{1}{2} \sqrt{\frac{L}{C}}$$


where R_C is the value required to achieve critical damping.

$$R_C = \frac{1}{2} \sqrt{\frac{10^{-3}}{10^{-4}}} = \frac{1}{2} \sqrt{10} = 1.581 \Omega$$

given that

$$R = 0.1 R_C = 0.1581 \Omega = 158.1 \text{ m}\Omega$$

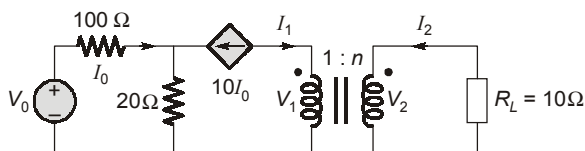Q.27 The voltage gain (magnitude) of the circuit shown below is _____. (Assume $n = 1/10$)



27. 3.125 (2.600 to 3.400)

Applying KVL in the left most loop,

$$\begin{aligned} V_0 &= 100 I_0 + 20 (I_0 - I_1) \\ &= 100 I_0 + 20 (I_0 + 10 I_0) \\ &= 100 I_0 + 220 I_0 \end{aligned}$$

$$I_0 = \frac{V_0}{320} \text{ A}$$

$$I_1 = -10 I_0 = -10 \frac{V_0}{320} = \frac{-V_0}{32}$$


$$I_2 = \frac{-I_1}{n} = \frac{V_0}{32} \times 10 = \frac{10 V_0}{32}$$

$$V_2 = -R_2 I_2 = (-10) \left(\frac{10 V_0}{32} \right) = \frac{-100}{32} V_0$$

$$\text{Voltage gain} = \frac{V_2}{V_0} = \frac{-100}{32} = -3.125$$

$$\left| \frac{V_2}{V_0} \right| = 3.125$$

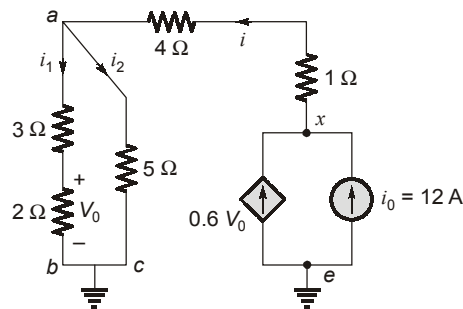Q.28 The potential at node 'x' with respect to 'e' is _____ V.



28. 225 (224.00 to 226.00)

Let the current be shown in the figure

$$i = 0.6 V_0 + 12$$

$$i = i_1 + i_2$$

Since branches *ab* and *ac* have identical resistance,

Hence, $i_1 = i_2$

and $i = 12 + 0.6 V_0 = 2i_1 = 2i_2$

$$V_0 = (i_1 \times 2) \text{ V}$$

$$i = 2i_1, \text{ we write}$$

$$i_1 = \frac{i}{2} = \frac{1}{2}(12 + 0.6 V_0)$$

and $V_0 = i_1 \times 2 = i_1 + 0.6 V_0$


$$V_0 = i_1 \times 2 = 12 + 0.6 V_0$$

Equation resistance across *xe* node is:

$$R_{xe} = (5 \parallel 5) + 4 + 1 = 7.5 \Omega$$

$$\begin{aligned} V_{xe} &= 0.6 V_0 \times 7.5 + 12 \times 7.5 \\ &= 18 \times 7.5 + 12 \times 7.5 \\ &= 225 \text{ V} \end{aligned}$$

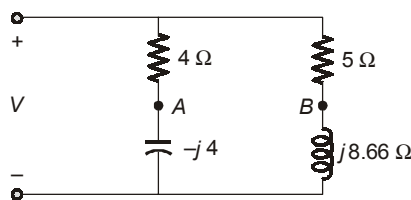
- Q.29** In the parallel circuit shown in figure, the applied voltage V (magnitude only) is _____ V, where $V_{AB} = 48.3 \angle 30^\circ$ V.



- 29. 50 (49.00 to 51.00)**
 By voltage division in 2 branches

$$\begin{aligned}
 V_{AX} &= \frac{-j4}{4-j4} V = \frac{1}{1+j} V \\
 V_{BX} &= \frac{j8.66}{5+j8.66} V \\
 V_{AB} &= V_{AX} - V_{BX} \\
 &= \left(\frac{1}{1+j} - \frac{j8.66}{5+j8.66} \right) V = \frac{1}{-0.268+j1} V \\
 V &= (-0.268+j1) V_{AB} \\
 &= (1.03 \angle 105^\circ) (48.3 \angle 30^\circ) \\
 &= 50 \angle 135^\circ V
 \end{aligned}$$

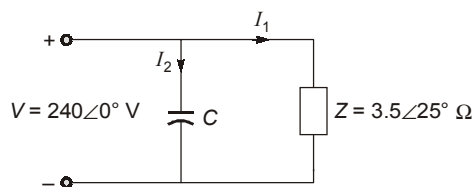- Q.30** _____ μ F capacitance C must be provided by the capacitor bank in the figure given below to improve the power factor to 0.95 lagging. Frequency is 50 Hz.



- 30. 113.5 (112.00 to 115.00)**

Before addition of capacitor bank,

$$\text{pf} = \cos 25^\circ = 0.906 \text{ lag}$$

$$I_1 = \frac{240 \angle 0^\circ}{3.5 \angle 25^\circ} = 68.6 \angle -25^\circ \text{ A}$$

$$\begin{aligned}
 S &= V_{\text{eff}} I_{\text{eff}}^* \\
 &= (240 \angle 0^\circ) (68.6 \angle 25^\circ) = 14921.45 + j6958
 \end{aligned}$$

After improvement, the triangle has the same P , but its angle is $\cos^{-1} 0.95 = 18.19^\circ$


From the triangle,

$$\frac{6958 - Q_c}{14921.45} = \tan 18.19^\circ$$

$$Q_c = 2053.52 \text{ VAR}$$

$$X_c = \frac{V_c^2}{Q_c}$$


$$X_c = 28.05 \Omega$$

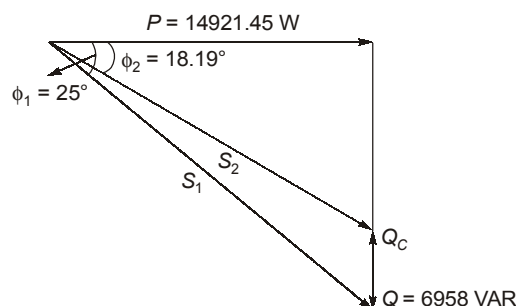

$$C = \frac{1}{2\pi \times 50 \times 28.05} = 1.135 \times 10^{-4}$$

$$= 113.5 \mu\text{F}$$

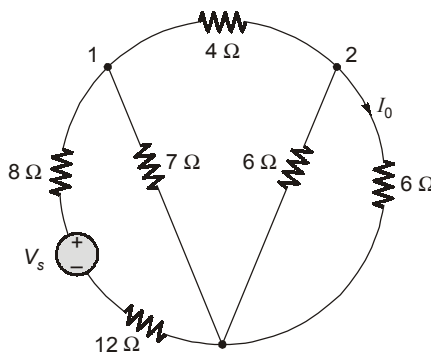Q.31 For the network shown below, the value of V_s is _____ V which makes $I_0 = 7.5$ mA.



31. 0.705 (0.680 to 0.730)

The node voltage method will be used and the matrix form of equation are

$$\text{Voltage at node 1} = V_1$$

$$\text{Voltage of node 2} = V_2$$

Applying KCL at node 1,

$$\frac{V_1}{20} + \frac{V_1}{7} + \frac{V_1}{4} - \frac{V_2}{4} = \frac{V_s}{20}$$

$$\frac{31}{70}V_1 - \frac{V_2}{4} = \frac{V_s}{20}$$

...(i)

Applying KCL at node 2,

$$-\frac{V_1}{4} + \frac{V_2}{4} + \frac{V_2}{6} + \frac{V_2}{6} = 0$$

$$\frac{7}{3}V_2 = V_1$$

...(ii)

From equation (i),

$$\frac{31}{70} \times \frac{7}{3}V_2 - \frac{V_2}{4} = \frac{V_s}{20}$$

$$V_2 = 0.0638 V_s$$

$$\text{From circuit, } I_0 = 7.5 \times 10^{-3} = \frac{V_2}{6} = \frac{0.0638 V_s}{6}$$

$$V_s = 0.705 \text{ V}$$

Q.32 A series RLC resonant circuit has a resonance frequency of 1.5 MHz and bandwidth of 10 kHz. If $C = 150$ pF, then the value of resistance R is _____ Ω .

32. 4.715 (4.500 to 5.000)

For a series resonance circuit

$$\text{Bandwidth } f_2 - f_1 = \frac{R}{2\pi L}$$

$$\text{Resonant frequency, } f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$L = \frac{1}{(2\pi f_0)^2 \cdot C}$$


$$R = 2\pi L \cdot (f_2 - f_1) = \frac{2\pi(f_2 - f_1)}{(2\pi f_0)^2 \cdot C} = \frac{f_2 - f_1}{2\pi f_0^2 \cdot C}$$

$$= \frac{10 \times 10^3 \times 10^{12}}{2 \times \pi (1.5 \times 10^6)^2 \times 150}$$

$$R = 4.715 \Omega$$

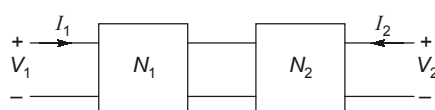Q.33 Two identical networks are connected in cascaded as shown in figure. Transmission matrix for one network

is $\begin{bmatrix} 1 & 4 \\ 3 & 2 \end{bmatrix}$. The value of Z_{12} is _____ (in ohms).



33. 11.11 (11.00 to 11.50)

If two networks are connected in cascaded, their transmission matrices are multiplied to get overall transmission matrix

$$T = \begin{bmatrix} 1 & 4 \\ 3 & 2 \end{bmatrix} \begin{bmatrix} 1 & 4 \\ 3 & 2 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 13 & 12 \\ 9 & 16 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$V_1 = 13V_2 - 12I_2 \quad \dots(i)$$

$$I_1 = 9V_2 - 16I_2 \quad \dots(ii)$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

Putting $I_1 = 0$ in equation (ii)

$$9V_2 = 16I_2$$

$$V_2 = \frac{16}{9}I_2$$

$$V_1 = 13V_2 - 12I_2 = 13 \times \frac{16}{9}I_2 - 12I_2$$

$$\frac{V_1}{I_2} = Z_{12} = 11.11 \Omega$$

○○○○